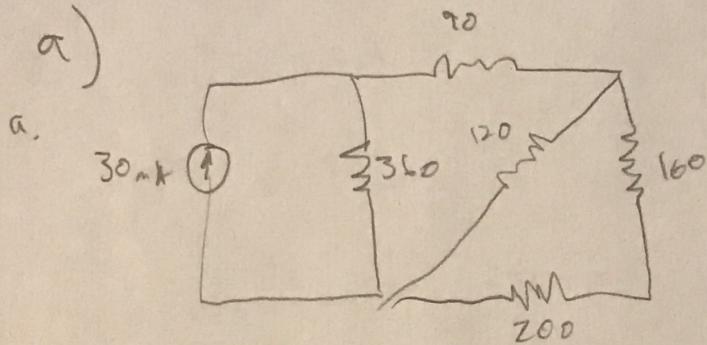


HW 3

Daren Liu

- 1) Voltage dividers require two or more resistors in series, while a current divider requires two or more resistors in parallel.

2) a)



$$200 + 160 = 360$$

$$\frac{1}{R_{eq}} = \frac{1}{360} + \frac{1}{120} = 90 \Omega$$

$$90 + 90 = 180$$

$$R_{eq} = \frac{1}{180} + \frac{1}{360} = \underline{\underline{120 \Omega}}$$

b.  $R_1 = 150 + 600 = 750$

$$R_2 = \left( \frac{1}{500} + \frac{1}{750} \right)^{-1} = 300$$

$$R_3 = 300 + 300 = 600 \Omega$$

$$R_4 = 750 + 250 = 1000 \Omega$$

$$R_5 = \left( \frac{1}{1000} + \frac{1}{1000} \right)^{-1} = 500 \Omega$$

$$R_6 = 500 + 100 = 600$$

$$R_{eq} = \left( \frac{1}{600} + \frac{1}{600} \right)^{-1} = \boxed{300 \Omega}$$

c.  $R_1 = 6 + 14 = 20$

$$R_2 = \frac{1}{\frac{1}{12} + \frac{1}{4} + \frac{1}{20} + \frac{1}{15} + \frac{1}{20}} = 2 \Omega$$

$$R_3 = 6 + 2 = 18 \Omega$$

$$R_4 = \left( \frac{1}{18} + \frac{1}{18} \right)^{-1} = 9 \Omega$$

$$R_{eq} = 8 + 9 + 10 = \boxed{27 \Omega}$$

d.  $R_1 = \left( \frac{1}{30} + \frac{1}{15} \right)^{-1} = 10 \Omega$

$$R_2 = 20 + 10 = 30 \Omega$$

$$R_3 = \left( \frac{1}{60} + \frac{1}{30} \right)^{-1} = 20 \Omega$$

$$R_4 = 10 + 20 = 30 \Omega$$

$$R_5 = \left( \frac{1}{60} + \frac{1}{80} + \frac{1}{30} \right)^{-1} = 16 \Omega$$

$$R_{eq} = 50 \Omega$$

$$b) V_a = (30\text{m})(120) = 3.6 \text{V}$$

$$P_a = (30)(3.6) = 108 \text{mW}$$

$$V_b = (50)(300) = 15 \text{V}$$

$$P_b = (50)(15) = 750 \text{mW}$$

$$I_c = \frac{144}{27} = 5.33 \text{A}$$

$$P_c = (5.33)(144) = 767.995 \text{W}$$

$$I_d = \frac{90}{50} = 1.6 \text{mA}$$

$$P_d = (80\text{m})(1.6) = 128 \text{mW}$$

$$3) a) \left( \frac{1}{30+120} + \frac{1}{75} \right)^{-1} = 50 \text{k}\Omega$$

$$V_1 = \frac{50 \cdot 240 \text{V}}{75} = 160 \text{V}$$

$$V_o = \frac{120}{150} \cdot 160 = 128 \text{V}$$

$$b) i = \frac{V}{R}$$

$$\frac{240}{(100)} \text{A} = 2.4 \text{mA}$$

$$V_o = \frac{120}{150} \cdot 180 = 144 \text{V}$$

c)  $V_o = 144$  with dependent voltage

$V_o = 128V$  without

dependent voltage source = higher voltage output

4) a)  $V_o = KV = \frac{R_2}{R_1 + R_2} V_S$

$$V_o = \alpha V_S = \frac{R_C}{R_1 + R_C} V_S$$

$$K = \frac{R_2}{R_1 + R_2} \quad R_1 = \frac{1-K}{K} R_2$$

$$\alpha = \frac{f_C}{R_1 + R_C} \quad f_1 = \frac{(1-\alpha)}{\alpha} f_C$$

$$R_2 = \frac{k-\alpha}{\alpha(1-k)} R_o$$

$$R_1 = \frac{k-\alpha}{\alpha k} R_o$$

b)  $R_1 = \left(\frac{0.05}{0.64}\right) R_o = \left(\frac{0.05}{0.64}\right) \cdot 34 \cdot 10^3 = 2.5 k\Omega$

$$R_2 = \left(\frac{0.05}{0.12}\right) \cdot 34 \cdot 10^3 = 14.167 k\Omega$$


c)  $P_{max_1} = \frac{(60 - 0.85)^2}{14167} = 183.6 \text{ mW}$

$$P_{max_2} = \frac{(60 - 0.8 \cdot 60)^2}{2560} = 57.60 \text{ mW}$$

$$d) P_{R_1} = \frac{60^2}{2500} = 1.44 \text{ W}$$

$$P_{R_2} = \frac{0^2}{14167} = 0$$

5)

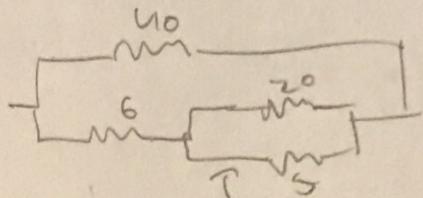

$$R_{eq} = \left( \frac{1}{4} + \frac{1}{10} \right)^{-1} = 8 \Omega$$

$$-125 + (i_g 2) - (i_g 8) = 0$$

$$10 i_g = 125$$

$$i_g = 12.5 \text{ A}$$

$$i_1 = \frac{U_0}{50} \cdot 12.5 = 10 \text{ A}$$

$$i_0 = \frac{5}{25} \cdot 10 = 2 \text{ A}$$

$$6) a) R_{volt} = 5000 \Omega$$

$$R_a = \left( \frac{1}{5} \cdot \frac{1}{45} + \frac{1}{5000} \right)^{-1} = 11.22$$

$$V_{max} = 11.22 \cdot 50 \text{ mF} = 561.23 \text{ mV}$$

$$b) R_{eq} = \left( \frac{1}{15} + \frac{1}{45} \right)^{-1} = 11.25 \Omega$$

$$V_{true} = 11.25 \Omega \cdot 50mA = 562.5 mV$$

$$\% \text{ error} = \left( \frac{561.23}{562.5} - 1 \right) \cdot 100 = -0.2258\%$$

$$7) R_a = \frac{(22 \times 20) + (20 \times 140) + (140 \times 22)}{22} = 287.3 \Omega$$

$$R_b = \frac{(22 \times 20) + (20 \times 140) + (140 \times 22)}{20} = 316 \Omega$$

$$R_c = \frac{(22 \times 20) + (20 \times 140) + (140 \times 22)}{140} = 45.1 \Omega$$

$$R_{eq1} = \left( \frac{1}{287.3} + \frac{1}{60} + \frac{1}{28} \right)^{-1} = 14.25 \Omega$$

$$\left( \frac{1}{316} + \frac{1}{60} \right)^{-1} = 60.6$$

$$\frac{1}{45.1 + 14.25} + \frac{1}{60.6} = 30 \Omega$$

$$i_S = \frac{240}{460} = 6 A$$

$$-240 + (i_0 \cdot 75) + 10i_S = 0$$

$$i_0 = 2.4 A$$

$$i_S - i_o - i_1 = 6 - 2.4 - i_1 = 0$$

$$i_1 = 3.6 A$$

$$(i_1 + i_2) + (140 \times i_2) - (i_0 \times 75) = 0$$

$$140i_2 = 100.8$$

$$i_2 = 0.72 \text{ A}$$

$$P_{140 \Omega} = 72.5 \text{ W}$$

$$8) \quad a) \quad R_1 = 70 \quad R_2 = 20 \quad R_3 = 40$$

$$R_a = \frac{(80)(20) + (20)(40) + (40)(80)}{80} = 70$$

$$R_b = \frac{(80)(20) + (20)(40) + (40)(80)}{20} = 240$$

$$R_c = \frac{(80)(20) + (20)(40) + (40)(80)}{40} = 140$$

$$R_{eq1} = \left( \frac{1}{56} + \frac{1}{140} \right)^{-1} = 40$$

$$R_{eq2} = \left( \frac{1}{210} + \frac{1}{20} \right)^{-1} = 52.5$$

$$R_{eq3} = 40 + 52.5 = 92.5$$

$$R_{eq4} = \left( \frac{1}{92.5} + \frac{1}{20} \right)^{-1} = 69.53$$

$$i_A = \frac{5}{44.04} = 11.36$$

$$i = (44.04 \cdot 10^{-3}) \left( \frac{280}{280+20} \right) = 33.1 \text{ mA}$$

$$i_0 = (33.1 \cdot 10^{-3}) \left( \frac{20}{280} \right) = 8.275 \text{ mA}$$

b)  $i_1 = i \left( \frac{140}{140+56} \right) = 23.64 \text{ mA}$

$$i_{80A} = (44.04 \cdot 10^{-3}) - (23.64 \cdot 10^{-3}) 20.4 \text{ mA}$$

$$i_{20A} = (8.275 \cdot 10^{-3}) - (23.64 \cdot 10^{-3}) = -15.365 \text{ mA}$$

$$i_2 = 20.4 \text{ mA} - (-15.365) = 35.765 \text{ mA}$$

$$P = 5(44.04 \cdot 10^{-3}) = 0.2202 \text{ W}$$

a)  $R_a = \frac{3R^2}{R} = 3R$

$$R_b = \frac{3R^2}{R} = 3R$$

$$R_c = \frac{R^2}{R} = 3R$$

$$R_{ab} = \frac{\frac{9R^3 + 2.25R^2}{4R}}{\frac{3R^2 + 15R}{4R}} = R_L$$

b)  $i_0 = \frac{i_1(3R)}{3R + 0.75R + 0.75R} = \frac{i_1}{1.5}$

$$V_o = (0.75R_L)(i_0) = \frac{1}{2} V_i \quad \frac{V_o}{V_i} = 0.5$$

$$10) \quad a) \quad V_a = \frac{V_{in} R_1}{R_0 + R_4 + \Delta R}$$

$$V_b = \frac{R_3}{R_2 + R_3} V_{in}$$

$$V_o = V_a - V_b$$

$$\frac{R_4}{R_0 + R_4} = \frac{R_3}{R_2 + R_3}$$

$$V_o = -\frac{\Delta R R_4}{(R_0 + R_4)^2} V_{in}$$

$$b) \quad \Delta R = 0.03 R_0$$

$$R_0 = \frac{R_2 R_4}{R_3} \approx 10000 \Omega$$

$$\Delta R = 0.03 (10000) = 300 \Omega$$

$$V_o = \frac{-(300)(500)}{(15000)} \cdot b = -8.1 \text{ mV}$$

$$c) \quad V_o = \frac{-(300)(500)}{(15300)(15000)} \cdot b = -7.9 \text{ mV}$$