


$$j) R_{ad} = 4//4 + 1 = 3 \Omega$$

$$R_{cd} = 3//6 = 2 \Omega$$

$$R_{ca} = 6 \Omega$$

$$V = IR$$

$$54 = i_s(6)$$

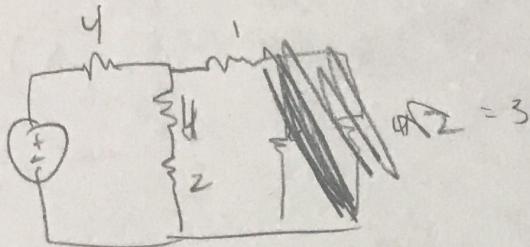

$$i_s = 9A$$

$$V_d = 54 - (9)(4) = 18 \quad | \boxed{V_a = 18} \quad | \boxed{V_d = 0}$$

$$\frac{V_b - V_a}{4} + \frac{V_b - V_d}{4} + \frac{V_b - V_a}{4} = 0$$

$$V_b - 18 + \frac{V_b}{4} + \frac{V_b}{4} = 0 \quad V_b \left(1 + \frac{1}{4} + \frac{1}{4}\right) = 18$$

$$\frac{V_c - V_a}{4} + \frac{V_c}{6} + \frac{V_c}{3} = 0$$

$$V_c \left(\frac{1}{4} + \frac{1}{6} + \frac{1}{3}\right) = \frac{18}{4}$$

$$| \boxed{V_b = 12}$$

$$| \boxed{V_c = 6}$$

$$I_c = \frac{V_a - V_c}{4} = \frac{18 - 6}{4} = 3A$$

$$54 - 18 - 6 = 30V$$

$$30 = i_o(6)$$

$$| \boxed{i_o = 5A}$$

$$2) \frac{V_1}{R_1} + \frac{V_1 - V_4}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} - i_{S2} = 0$$

$$\frac{V_4}{R_1} + \frac{V_4 - V_5}{R_4} + i_{S2} + \frac{V_5}{R_5} + \frac{V_5}{R_6} - i_{S3} = 0$$

$$V_2 - V_1 = V_{S1} \quad V_2 - V_3 = V_{S2}$$

$$V_4 - V_5 = V_{S3}$$

3) Supermesh in $i_1/i_2/i_3$, one in i_4/i_5





$$i_1 R_1 + i_{S1} + R_5(i_3 - i_4) + R_6 i_3 + i_{S2} - i_{S1} + R_2 i_2 - i_{S2} = 0$$

$$R_5(i_4 - i_3) + R_3 i_4 - R_4 i_5 + R_7 i_4 = 0$$


$$i_5 - i_4 = 4i_x \quad i_x = i_2$$

$$= 4i_2$$

$$4) V=IR$$

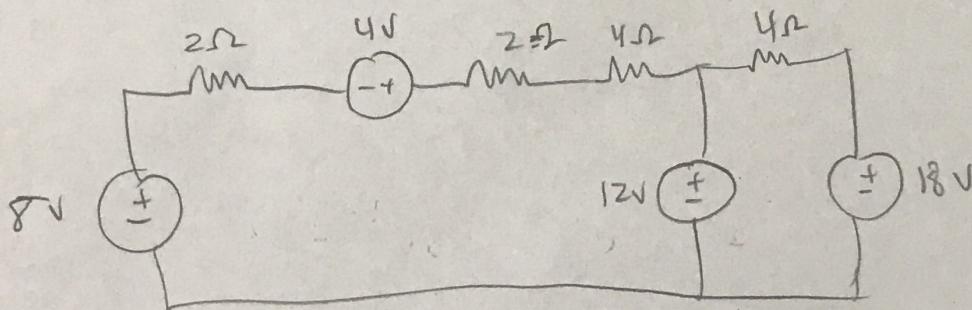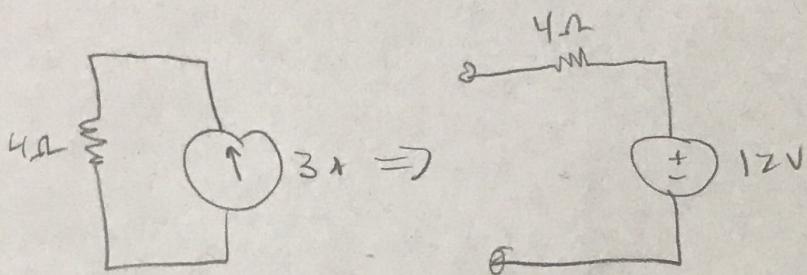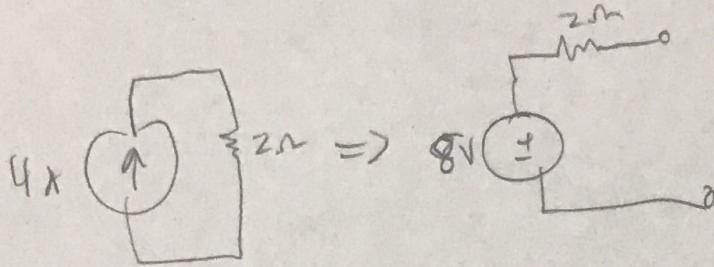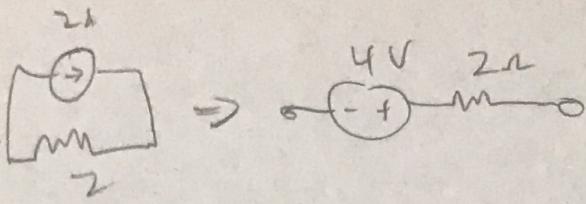


18 - 12

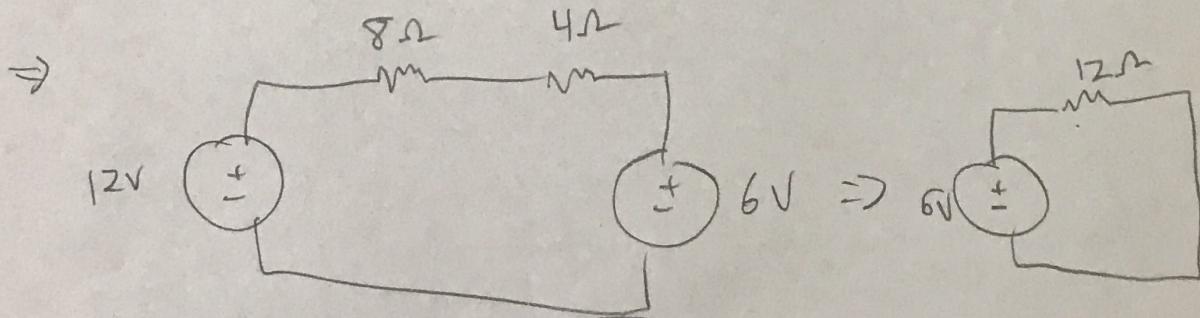

$$6 = 12(I) \quad \boxed{I_0 = 0.5 \text{ A}}$$


5) V_o)

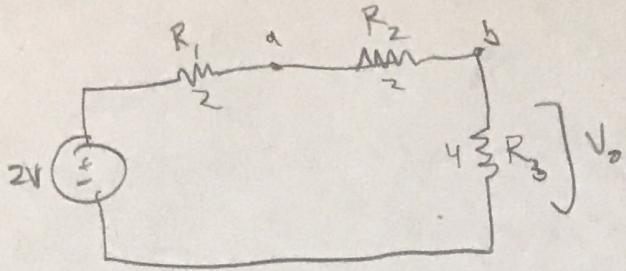

$$V_o = \frac{R_3}{R_1 + R_2 + R_3} (2)$$


$$= \frac{4}{8} (2) = 1 \text{ V}$$

i3)

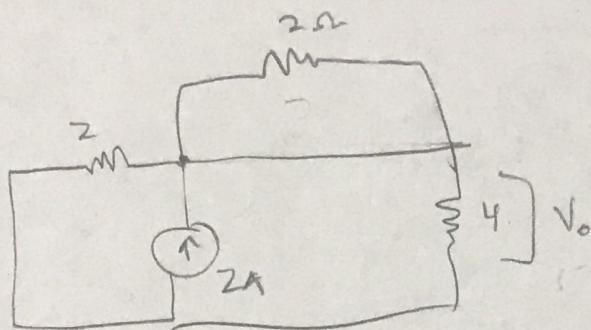


$$R_{eq} =$$

$$V = IR$$

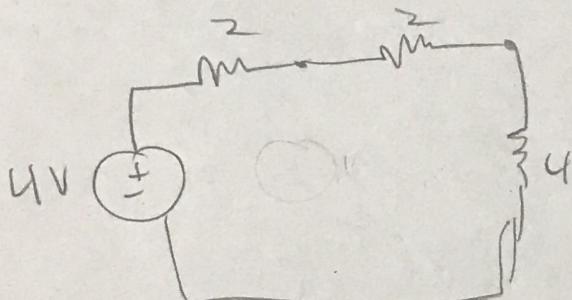

$$V_o = \frac{4}{4+2+2} (4) = 2 \text{ V}$$


V_o)

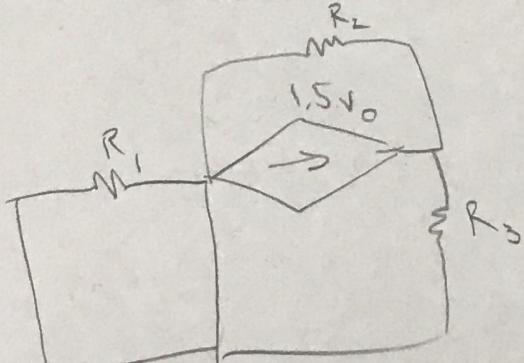

$$V = IR$$

$$1.5V_o \cdot 2 =$$

⇒

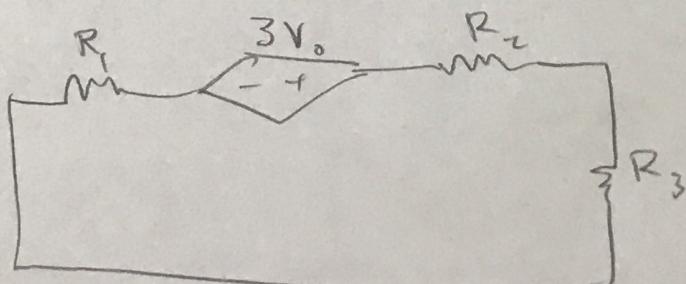

$$R_{eq} = 8 \Omega$$

$$3V_o = 8$$


$$I = \frac{3V_o}{8}$$

$$-3V_o + I_o(R_1 + R_2 + R_3) =$$

$$\frac{3V_o}{8} \cdot 4 = \frac{3}{2}V_o$$


$$V_o = 1 + 2 + \frac{3}{2} = 4.5 \text{ V}$$

6)

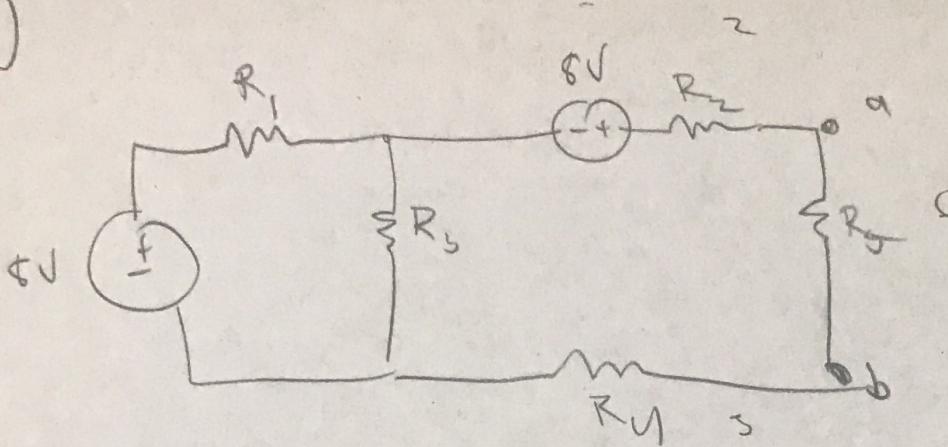

$$V_{OC} = V_{AB} = i_5 R_5$$
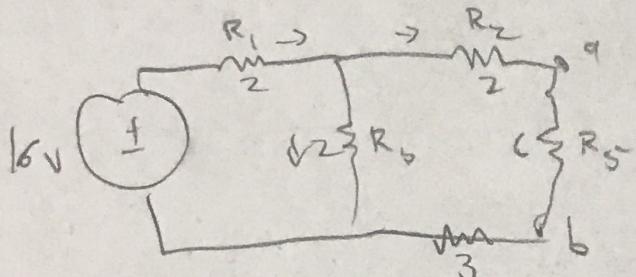
$$\left(\frac{1}{R_1} + \frac{1}{R_2}\right)^{-1} + 2$$



$$R_{eq} = 3.692\Omega$$

$$16 = I(3.692)$$

$$I_S = 4.333$$

$$I_S = I_3 + I_5$$

$$-16 + (4.333)(z) + (i_3)(z)$$



$$I_3 = \frac{2}{3}$$

$$i_3 = 3.666$$

$$V_{OC} = \left(\frac{2}{3}\right)(6) = 4V$$



$$V = IR$$
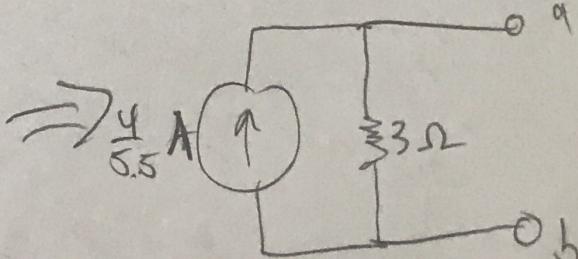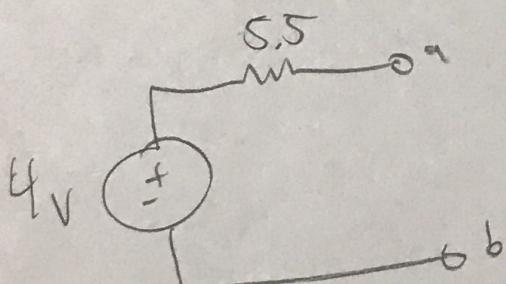
$$R_{th} = R_{eq} = \left(R_1 \parallel R_3 + R_4\right) + R_2 \parallel R_5 = 5.5$$




$$I = \frac{V}{R}$$

7)

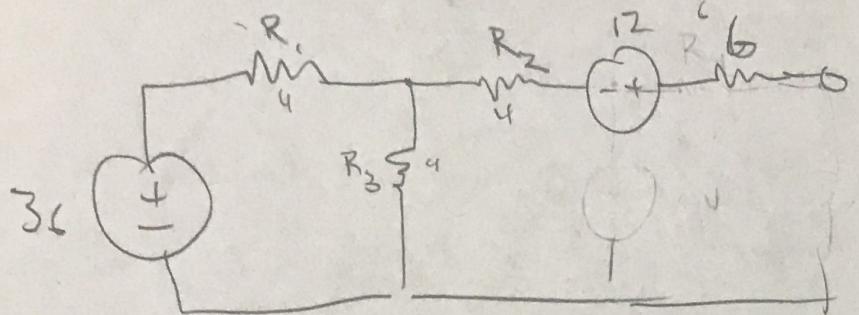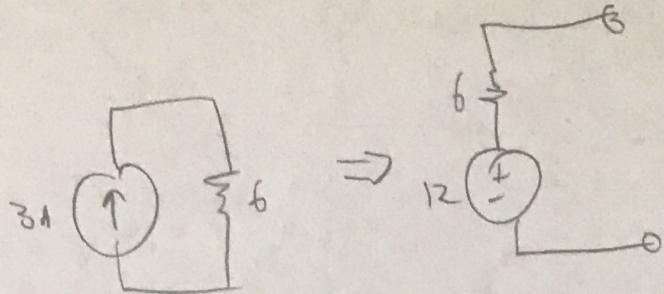 V_{oc}

$$P_{max} = \frac{(V)^2}{4R_{th}}$$

$$V_g = 48$$

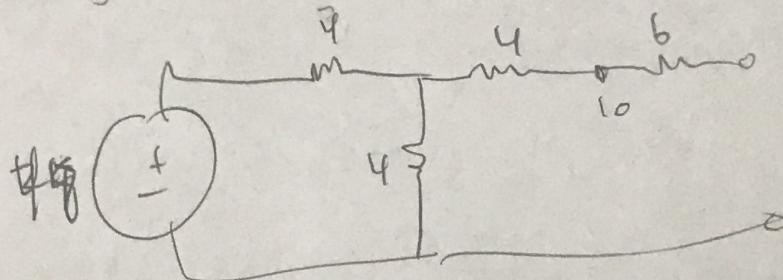

$$R_{eq} = 40/14 = 2.857 + 4 = 6.857$$

$$P_{max} = \frac{44^2}{4(6.857)} = \boxed{336 \text{ W}}$$

8)

$$\frac{V_n - V_a}{R_a} + \frac{V_n - V_b}{R_b} + \frac{V_n}{R_j} + \frac{V_n - V_o}{R_f} = 0$$


$$V_n = V_p = V_c$$

$$V_p = V_c$$

$$\frac{V_c - V_a}{R_a} + \frac{V_c - V_b}{R_b} + \frac{V_c}{R_j} + \frac{V_c - V_o}{R_f} = 0$$

$$V_o = R_f \left(\frac{V_c}{R_f} + \frac{V_c}{R_j} + \frac{V_c - V_b}{R_b} + \frac{V_c - V_a}{R_a} \right)$$

9) Capacitor is an open circuit $+ < 0$

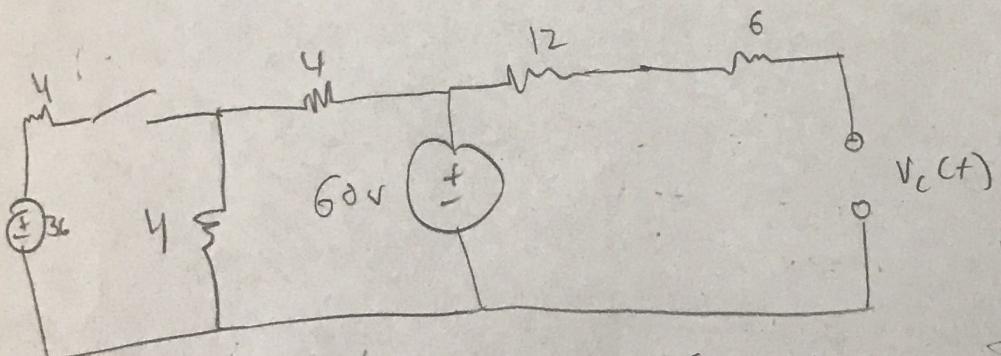


$$-60 + i_o(12 + 6) = 0$$

$$i_o = \frac{10}{3} A$$

$$V_c(0) - 60 + i_o(18) = 120 V$$

$$V_o(t) = \frac{\frac{10}{3}}{6} = 0.555 V$$

10)

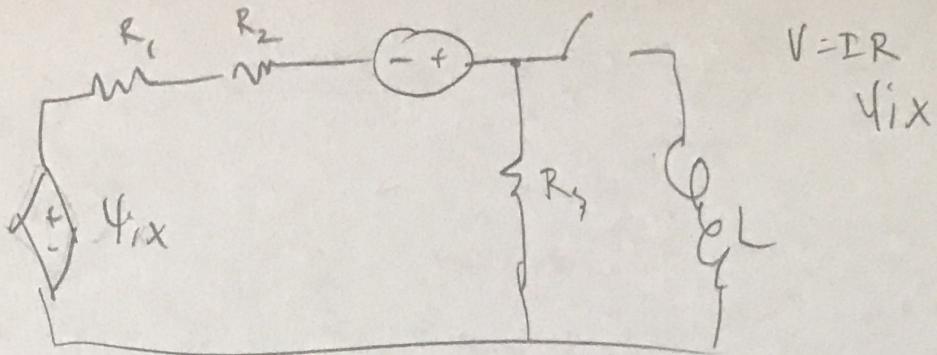

$$V = IR$$

$$\psi_{ix}$$

$$R_{12} \neq 6\Omega$$

$$I(0) = \frac{V_b}{R_b} + \frac{V_b}{R} =$$

$$11) \quad Z_C = \frac{1}{j\omega(\frac{1}{L})} = \frac{4}{j} \quad i_S = 3\cos(t) \quad I_S = 3 < 0^\circ$$

$$W = 1$$

$$Z_{R2} = 2$$

$$Z_{R1} = 4$$

$$Z_L = j\omega(3) = 3j$$

$$i_b = i_x + i_r$$

$$Z_{eq} = (Z_{R2} + Z_C) // (Z_{R1} + Z_L) = (2 + \frac{4}{j}) // (4 + 3j)$$


$$V_{dc}(t) = 0.5i_x$$

$$\frac{2j+4}{j} // (4+3j)$$

$$i_x = i_s - i_r$$

$$\left(\frac{j}{2j+4} + \frac{1}{4+3j} \right)^{-1}$$

12) V_{S1})

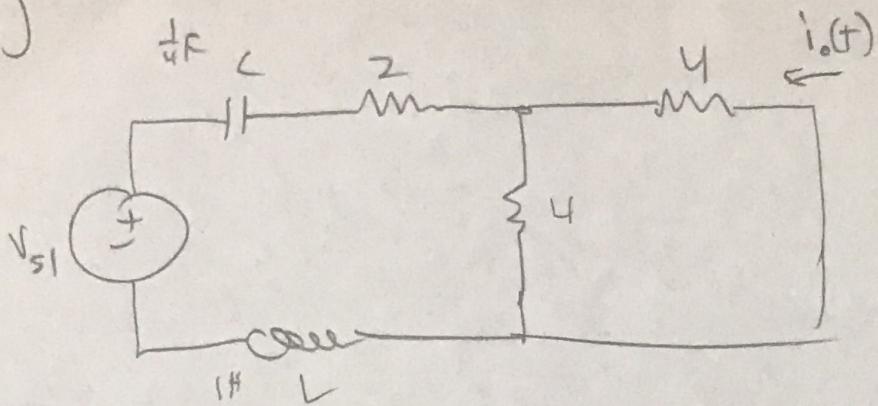


$$V_{S1} = 8 \cos(2t) = 8 \angle 0^\circ \quad \omega = 2$$

$$\begin{aligned} Z_{C1} &= \frac{1}{j(2)(\frac{1}{4})} \\ &= \frac{2}{j} \end{aligned} \quad Z_{L1} = j(2)(1) = 2j$$

$$-8 \cos(2t) + \frac{2}{j} + 2 + 4 + 2j = 0$$

$$Z_{eq} = \left(\frac{2}{j} + 2\right) + (4 \parallel (4 + 2j))$$

$V_{S2})$

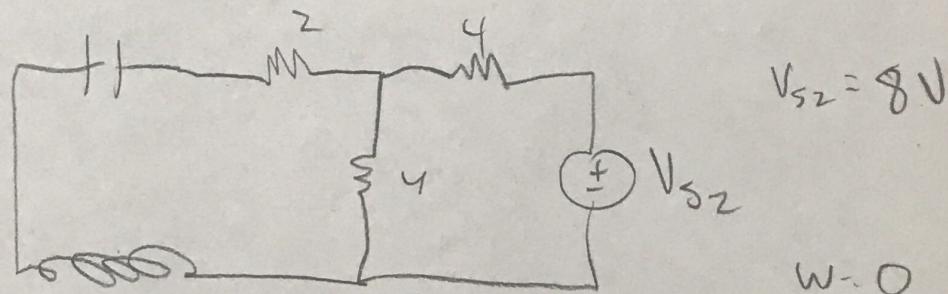


$$V_{S2} = 8V$$

$$\omega = 0$$

$$Z_{C2} = \infty \quad Z_{L2} = 0 \quad V = IR$$

$$Z_{eq} = 5.333$$

$$\frac{8}{5.333} = \boxed{1.5A}$$

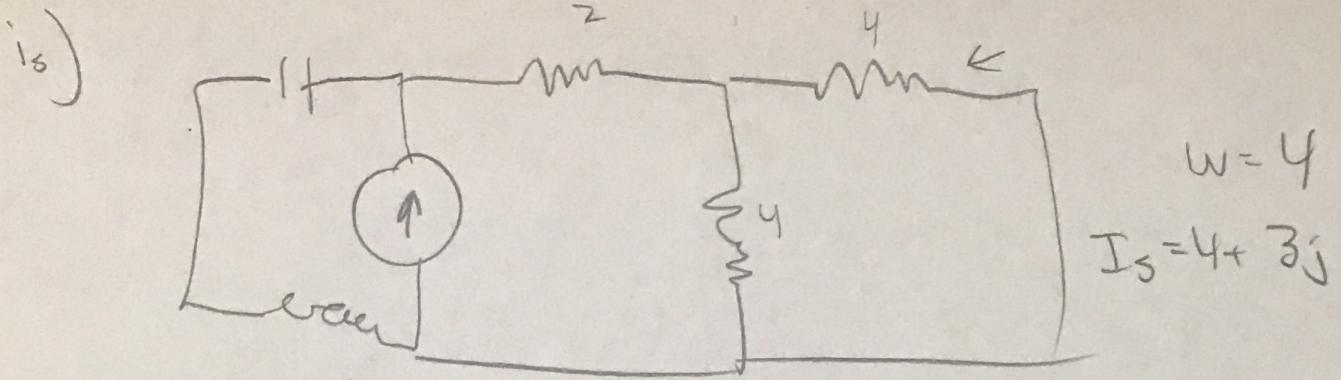

$$Z_C = \frac{1}{j(4)(\frac{1}{j})} = \frac{1}{j} \quad Z_L = j(4)(1) = 4j$$