

HW 4 set 2

Daren Liu

1) 4.63

a)

$$V = IR = 40 \text{ V}$$

$$R = 40 + 4 + 6 = 50 \Omega$$

$$V = 520 - 40 = 480 \text{ V}$$

$$U_0 = 480 \cdot \frac{250}{50+250} = 400 \text{ V}$$

$$I_0 = \frac{400}{250} = 1.6 \text{ A}$$

b) $P_{520V} = 520 \cdot 1.6 = \boxed{832 \text{ W}}$

c) $P_{1A} = 40 \cdot (-1.6) = \boxed{-64 \text{ W}}$

d) $R_{eq} = 250 + 50 = 300 \Omega$

$$P_{AB} = (1.6)^2 \cdot 300 = \boxed{768 \text{ W}}$$

2) 4.17

$$V = (3)(150) = 450 \text{ V}$$

$$450I_1 - 40I_2 = 300$$

$$-40I_1 + 200I_2 = -450$$

$$200I_1 = 1050$$

$$I_1 = 5.25 \text{ A} \quad I_2 = -1.2 \text{ A}$$

$$V_{th} = 10(-1.2) + 8(5.25) = 30 \text{ V}$$

$$R_{th} = \frac{50(150)}{50+450} = 15 \Omega$$

3) b. 74

$$\frac{V_1 - 100}{2500} + \frac{V_1}{625} - 10^{-3} V_a = 0$$

$$\frac{V_a - 5000i}{4000} + \frac{V_a}{6000} = 0$$

$$\left(\frac{1}{2400}\right)V_a = \frac{5}{4} i$$

$$i = -\frac{1}{2500}V_1 + \frac{1}{25}$$

$$V_1 = 50V \quad V_a = 60V \quad i = 0.02A$$

$$(V_{th} = 60V)$$

$$i_{sc} = \frac{5000i}{4000} = \frac{5000 \cdot \frac{100}{2500 \cdot 625}}{4000} = 0.04A$$

$$R_{Th} = \frac{V_{th}}{i_{sc}} = \frac{60}{0.04} \approx 1.5k\Omega$$

$$\frac{V - 250i_x}{200} - 1.5i_x + \frac{V}{750} - 1 = 0$$

$$i_x = \frac{V}{750}$$

$$3V - V - 3V + 2V = 1500 \quad V = 1500V$$

$$i_x = 2A$$

$$R_N = \frac{1500V}{1A} = 1500\Omega$$

5) f2)

a)
$$\frac{(5000)(1600 + \frac{2400+4800}{2400+4800} + 1800)}{5000 + 1600 + \frac{(2400+4800)}{2400+4800} + 1800} = 2500 \Omega$$

$$R_o = R_{th} = 2500 \Omega$$

b) $7200I_1 = 4800I_2 = 60$

$$4800I_2 - 4800I_1 + 8400I_3 = 0$$

$$I_2 - I_1 = 0.015$$

$$I_1 = 19.4 \text{ mA} \quad I_2 = 16.6 \text{ mA} \quad I_3 = 1.6 \text{ mA}$$

$$V_{Th} = 5000(i_3) = 8 \text{ V}$$

$$P_{max} = \frac{8^2}{4(2500)} = 6.4 \text{ mW}$$

c) $P = \left(\frac{V_{th}}{R_o + R_{th}} \right)^2 R_o = \left(\frac{8}{2700 + 2500} \right)^2 (2700) = 16.39 \text{ mW}$

$$= 16.39 \text{ mW}$$

6) a) $R_{th} = 1866.67 \Omega$

b) $I_o = \frac{60}{2} = 30 \text{ mA}$

$$P = 30^2 \cdot 1866.67 = 1.68 \text{ W}$$

$$c) I_1 = \frac{V_1}{2k} \quad I_2 = \frac{V_1 - V_2}{2} \quad i_2 = \frac{280 - V_2}{2}$$

$$224 = 28V_1 - V_2 \quad I_3 = \frac{V_2}{5.6}$$

$$I_0 = \frac{V_2}{1866.67}$$

$$i_A = \frac{280 - 100}{2} = 90 \text{ mA}$$

$$V_1 = 100 \text{ V} \quad V_2 = 56 \text{ V}$$

$$280 \cdot 90 \cdot 10^{-3} = 25.2 \text{ W}$$

$$0.2 \cdot i_2(V_1 - V_2) = 0.2 \cdot 90 \cdot 10^{-3} (100 - 56) = 0.792 \text{ W}$$

$$P_T = 25.2 + 0.792 = 25.992 \text{ W}$$

$$\rho \% = \frac{1.68}{25.992} \cdot 100 = 6.46\%$$

$$d) R = 1800 \Omega$$

$$e) i_A = \frac{280 - V_1}{2} = \frac{280 - 91.63}{2} = 90.18 \text{ mA}$$

$$280 \cdot 90.18 \cdot 10^{-3} = 25.28 \text{ W}$$

$$0.2 \cdot 90.18 \cdot (100.63 - 54.98) = 0.805 \text{ W}$$

$$P_T = 25.25 \cdot 0.805 = 20.055 \text{ W}$$

$$P_{1800\Omega} = \frac{V_2^2}{1800} = 1.671 \text{ W}$$

$$\frac{1.671}{20.055} \cdot 100 = 6.32\%$$

7) a)

$$i_3 = -(i_2 + i_1)$$

$$-124i_2 + 12i_3 + 4i_1 - 8i_2 = 0$$

$$i_3 = \frac{-116i_2 - 128i_1}{12}$$

$$i_1 = \frac{100 - 41.33i_2}{57.33}$$

$$i_2 = -4.1 A$$

$$i_1 = \frac{100 + 169.4665}{57.33} = 4.7 A$$

$$V_{th} = -i_3(80) = (i_2 + i_1)(80)$$

$$V_{th} = (4.7 - 4.1)(80) = 48 V$$

$$i_3 = \frac{2i_2 - 1}{3} \quad i_1 = \frac{300 - 8i_2}{56}$$

$$i_2 = 2.5159 \quad i_1 = 4.0977$$

$$i_N = 4.0977 + 2.5159 = 7.5136$$

$$P_{th} = \frac{48}{75136} = 6.3884$$

b) $V = (48) \left(\frac{6.3884}{2(6.3884)} \right) = 24$

$$P_{max} = \frac{48^2}{6.3884} = 360.1537 W$$

c) $i_4 = \frac{80i_1 - 6.3884}{86.3884}$

$$i_3 = \frac{-13.1698i_1 + 1.1698i_2}{12}$$

$$i_1 = \frac{100 + 305i_2}{21.5261}$$

$$i_2 = -0.9771A \quad i_1 = 4.9025$$

$$i_3 = -5.4659$$

$$P_V = 100 \cdot 4.9025 = 490.25 \text{ W}$$

$$\% P = \frac{360.6537}{490.25} \cdot 100 = 73.57\%$$

d) R_0 , close to 6.3864

9) 91)

$$a) \quad I_1 + I_2 + I_3 + I_4 + I_5 = 0$$

$$\frac{V_1}{16} + \frac{V_1 - 180}{20} + \frac{V_2}{10} - 0.1V_A + \frac{V_2 - 180}{10} = 0$$

$$V_A = 2 \cdot I_5 = 2 \cdot \frac{V_1 - 180}{10}$$

$$V_1 = 5V_A = 180$$

$$V_1 = 180V \quad V_A = -20V$$

$$V_{Th} = 190 + V_2 = 160 \text{ V}$$

$$\frac{190i_1 - 720}{16} + \frac{192i_4 - 720 - 180}{20} + \frac{8i_4 - 720}{10} - 0.1(-180)$$

$$+ (i_4 - 90) = 0$$

$$i_d = 0 \quad I_{sc} = 10$$

$$R_{Th} = \frac{160}{10} = 16 \Omega$$

$$b) I_0 = \frac{110}{16+16} = 5$$

$$P_{R_0} = I^2 (16) = 25 \cdot 16 = 400 \text{ W}$$

$$c) I_5 = \frac{V_2 - V_0}{8} = \frac{V_2 - 80}{8}$$

$$\frac{V_1}{16} + \frac{V_1 - 180}{20} + \frac{V_2}{10} + 10 + (i_0 - q_0) + \frac{V_2 - 80}{20} = 0$$

$$V_1 = 640 \text{ V} \quad V_2 = -280 \text{ V}$$

$$I_5 = -(I_2 + i_2)$$

$$I_2 = -\frac{100}{2} = -50 \text{ A}$$

$$I_2 = \frac{640 - 180}{20} = 23 \text{ A}$$

$$P_{180V} = 180 \cdot 27 = 4860 \text{ W}$$

$$d) \begin{aligned} a_3 & -q_0 i_1 - 100 i_2 + 230 i_3 = 0 \\ 125 i_2 - 100 i_3 & = 0 \end{aligned}$$

$$10 i_1 - 90 i_3 = -135$$

$$i_a = -2.25 \text{ A} \quad V_a = -90 \text{ V}$$

$$-\frac{V_b}{60} + \frac{-V_b}{30} + 16 = 0$$

$$3V_b = 1080$$

$$(V_b = 360 \text{ V})$$

$$V_1 = 441.6 \quad V_2 = 192 \text{ V}$$

$$i_b = \frac{192}{40} = 4.8 \text{ A}$$

$$V = V_a + V_b = -90 + 360 = 270 \text{ V}$$

$$i_o = -2.25 + 4.8 = 2.55 \text{ A}$$

$$(10) \quad -90 + 2000(i_1 - i_3) + 2.5 V_b = 0$$

$$V_b = 1000 i_3$$

$$2000i_1 + 500i_3 = 90$$

$$6000i_2 - 6500i_3 = 0$$

$$-2000i_1 - 4000i_2 + 2000i_3 = 0$$

$$i_1 = 0.038 \text{ A}$$

$$i_2 = 0.0309 \text{ A}$$

$$i_3 = 0.028$$

$$i = i_1 - i_2 = 0.038 - 0.0309 = 7.2 \text{ mA}$$

$$2000i_1 + 500i_3 = 0$$

$$5000i_2 - 6500i_3 = -40$$

$$-2000i_1 - 4000i_2 + 2000i_3 = 0$$

$$i_1 = 2.1 \text{ mA} \quad i_2 = -0.0158 \quad i_3 = 8.42 \text{ mA}$$

$$i'' = i_1 - i_2 = 0.0179$$

$$2.7 \cdot 10^{-3} + 0.0179 = \boxed{25 \text{ mA}}$$