

Santa Clara University

Department of Electrical and Computer Engineering

No. _____ Daren Liu Submitted on: 10/15/20
Name (please print)

• Include this page with Homework


• Write Name and Page Number on each page

ELEN 153
Fall 2020


Problem Set #3

Due: 10-15-2020, Thursday, 12:00 pm

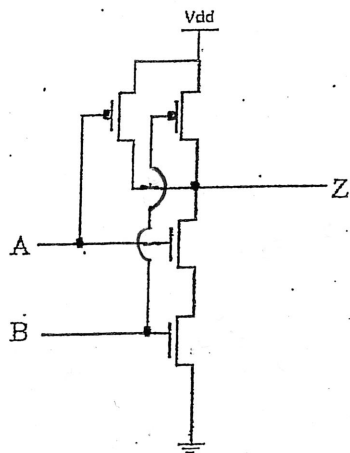
1. a) Express output(s) as logical functions of input variables for the circuits in Figs. 1-7.
b) Draw CMOS PDN and PUN circuits to implement the logic diagrams in Figs. 8-11.
- _____




1 ③

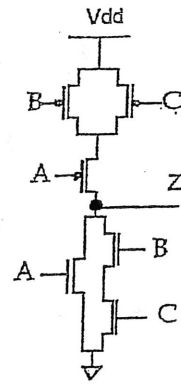


2 ⑤

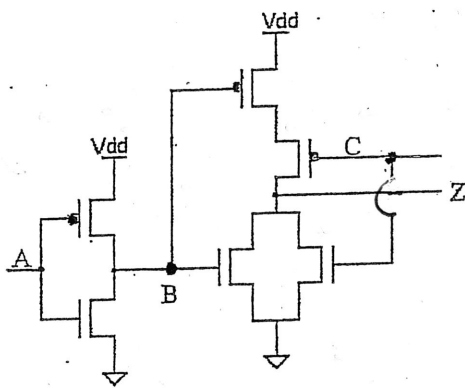


3 ⑥

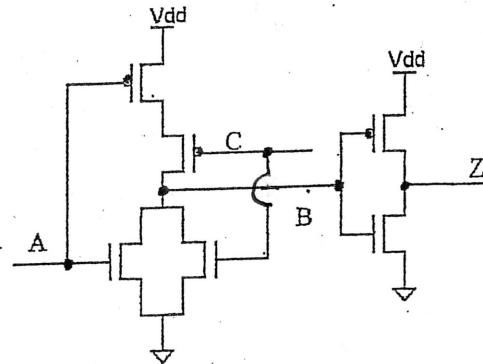

4 ⑧

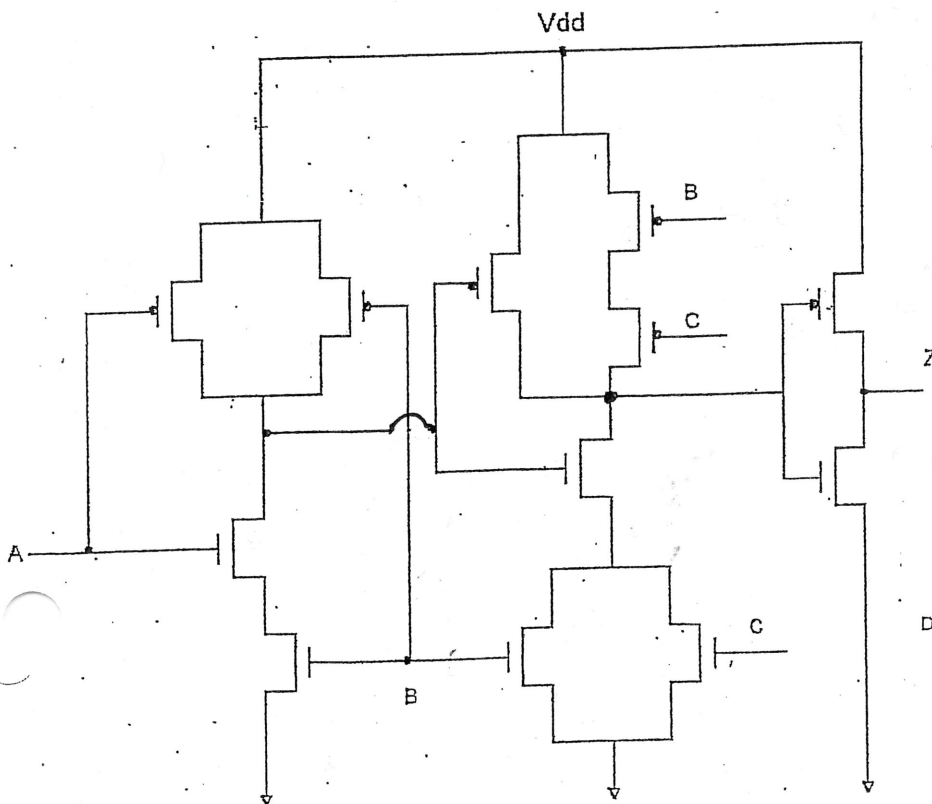

⑩

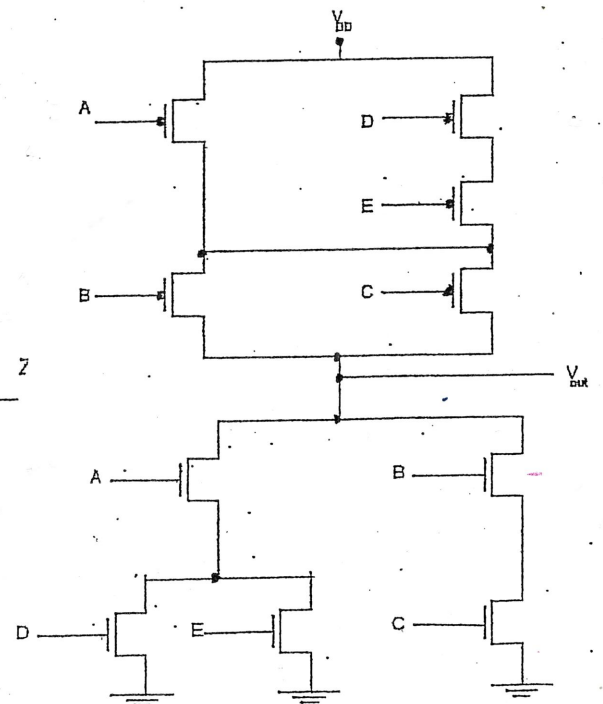


6 ⑩

1)

Lin ①

$$Z = (\overline{A \cdot B}) + (\overline{A \cdot B})$$


$$= (\overline{A \cdot B})$$

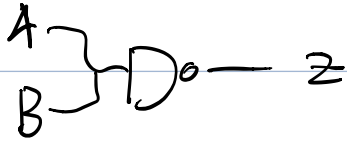

A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0


$$2) \quad ((B \cdot C) + A) + (\overline{A + (B \cdot C)})$$

$$= \overline{A + (B \cdot C)}$$

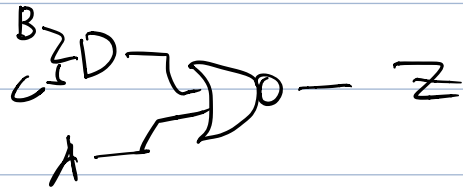

$$3) \quad (\overline{B + C}) + (\overline{B + C}) \quad \overline{A} = B$$
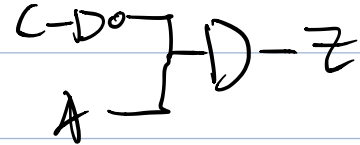
$$\overline{B \cdot C} + \overline{B \cdot C} = \overline{B \cdot C} = A \cdot \overline{C}$$




4)

$$\overline{(A + C) + (A + C)} = \overline{A + C}$$

$$B = \overline{A + C} \quad \overline{B} = A + C$$


$$Z = A + C$$

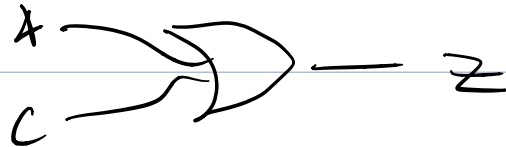

$$5) \quad (\overline{A \cdot B}) + (\overline{A \cdot B}) = \overline{A \cdot B}$$

$$\overline{(B + C) \cdot (\overline{A \cdot B})} = (B + C) \cdot (\overline{A \cdot B})$$


Liu (2)

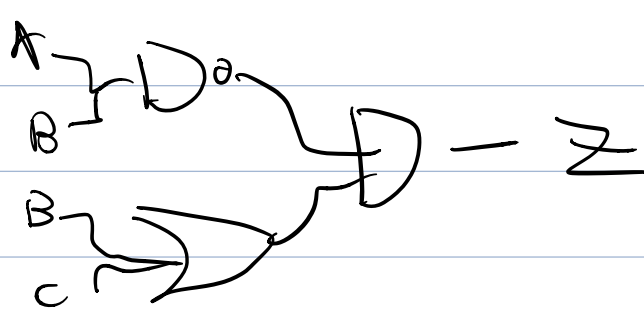

$$6) \quad \overline{(A+B)} + (D+E + (\overline{A+B}) + C)$$


$$\left((\overline{AD}) + (\overline{AE}) \right) + BC$$


$$= \overline{(BC + A(D+E))}$$

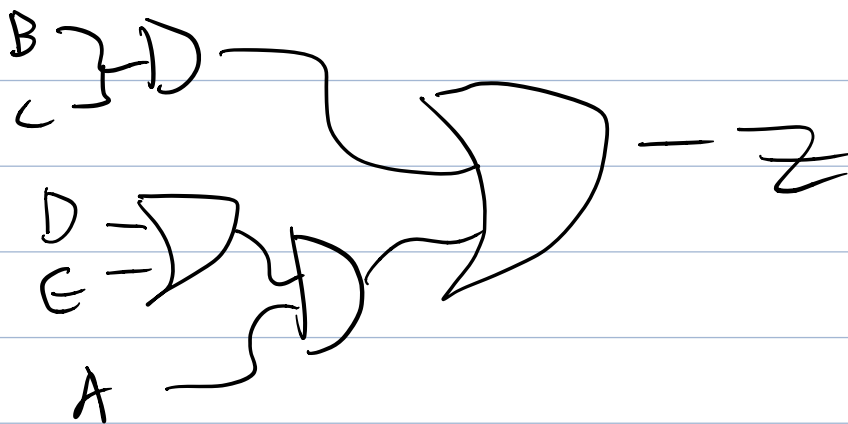


$$7) \quad X = (A+B)(C) + AB$$

$$Y = \overline{X}(A+B+C) + XABC$$

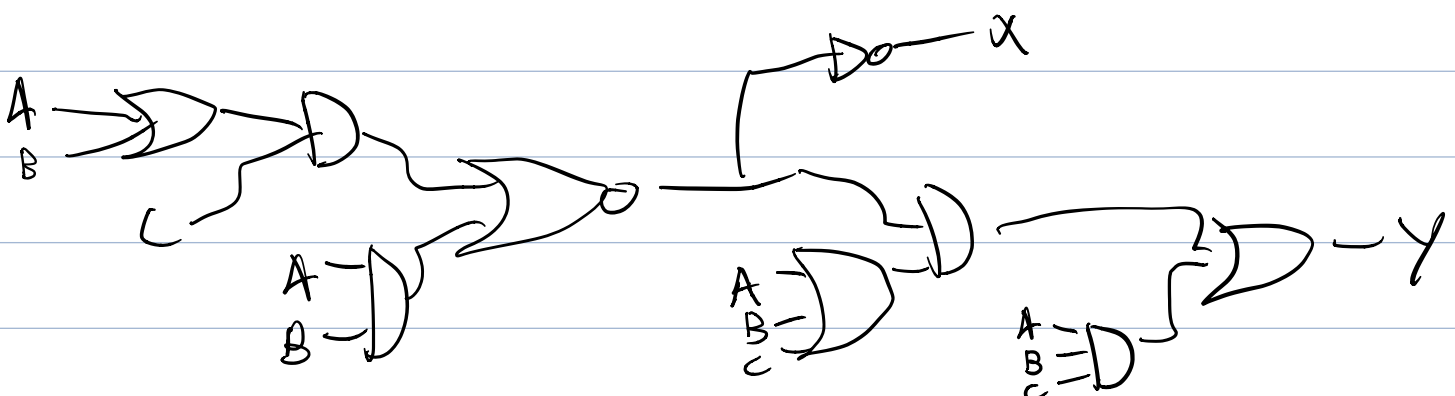

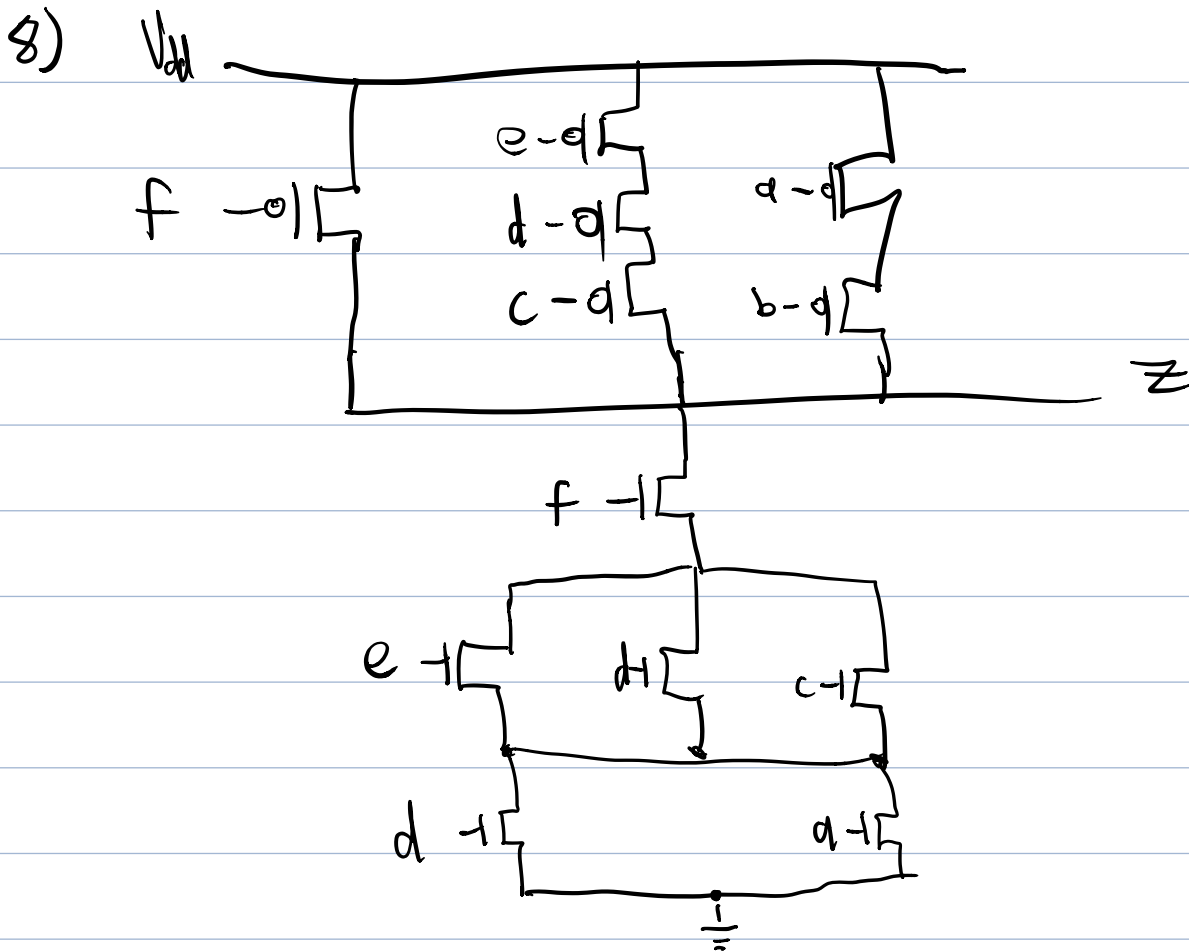


9)

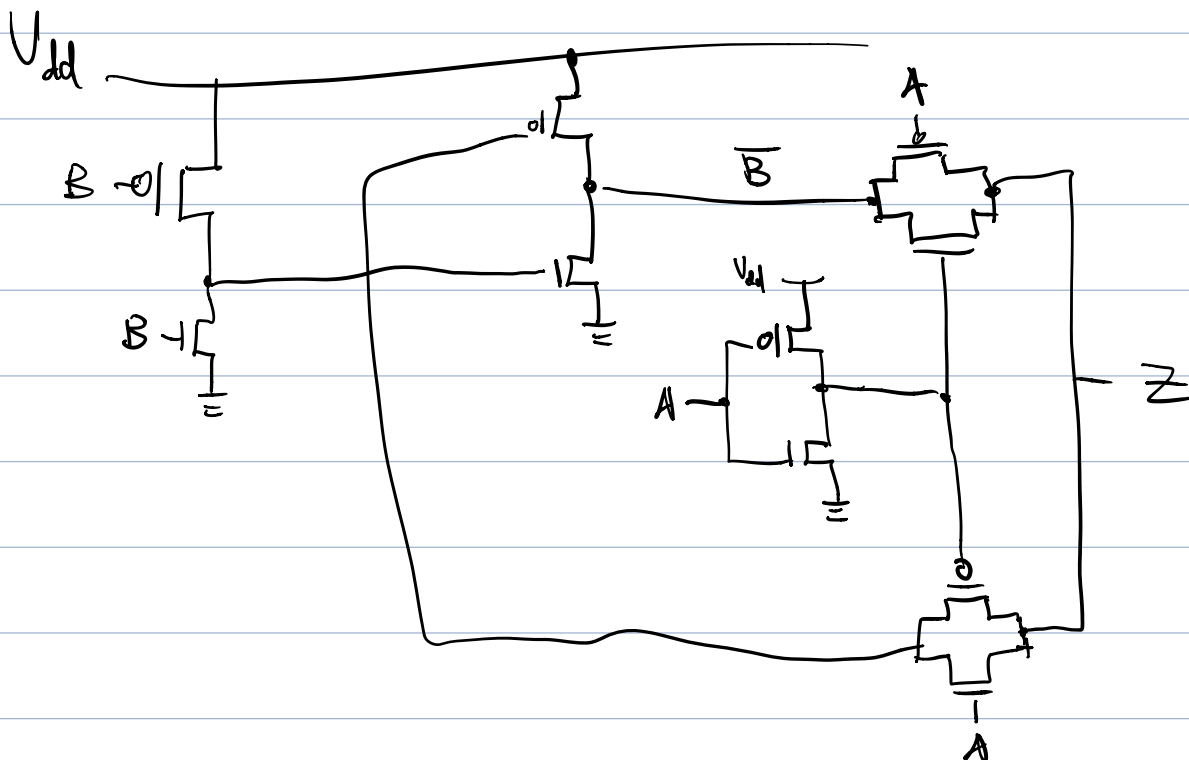

10)

Liu (4)

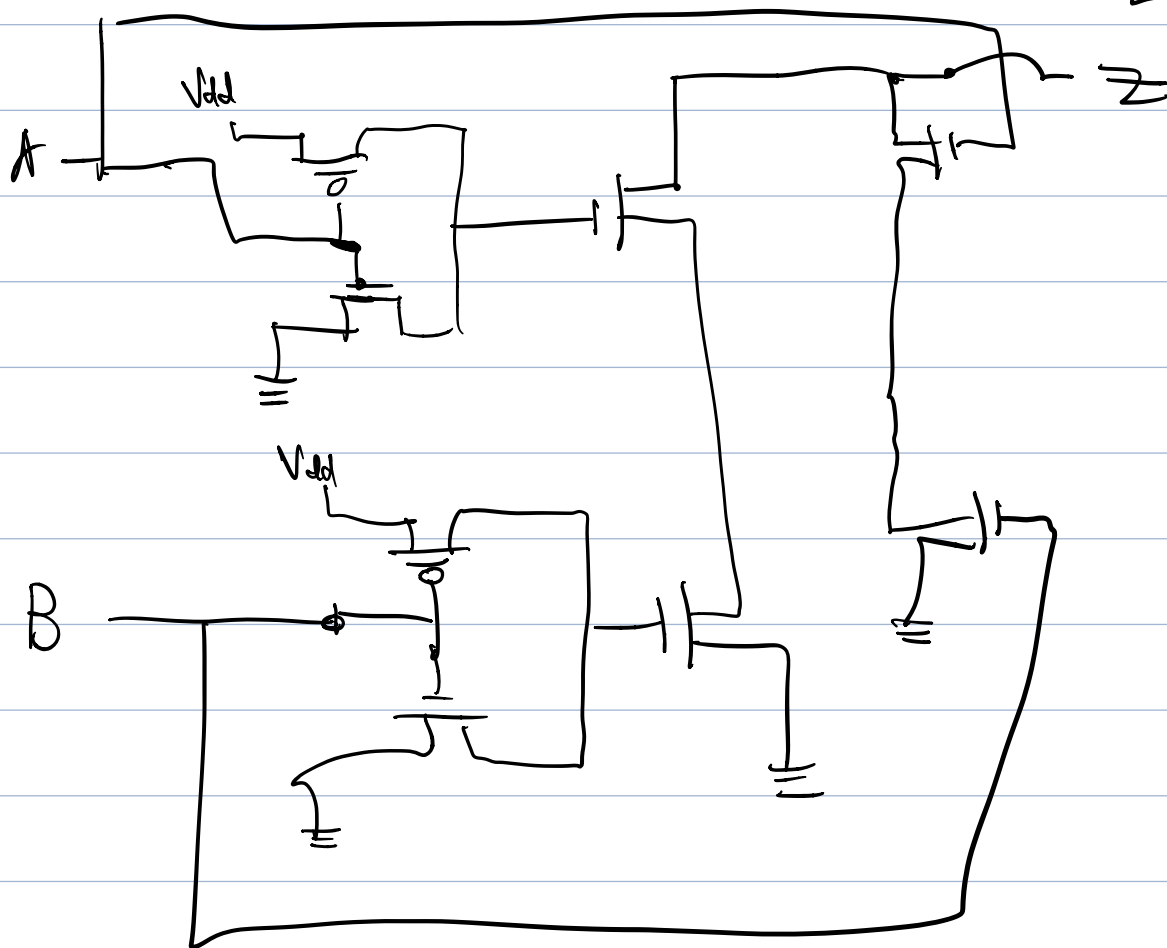

11)

