

HW 4. Set #1

1) All circuits have nodes, but not all circuits have two currents.

It can use less equations

$$2) \frac{V_1 - 144}{4} + \frac{V_1}{10} + \frac{V_1 - V_2}{80} = 0$$

$$V_1 \left(\frac{1}{4} + \frac{1}{10} + \frac{1}{80} \right) + V_2 \left(-\frac{1}{80} \right) = \frac{144}{4}$$

$$29V_1 - V_2 = 288 \quad (1)$$

$$\frac{V_2 - V_1}{80} + 3 + \frac{V_2}{5} = 0$$

$$V_1 \left(-\frac{1}{80} \right) + V_2 \left(\frac{1}{80} + \frac{1}{5} \right) = 3$$

$$-V_1 + 17V_2 = 240$$

$$17(29V_1 - V_2) = 17(240)$$

$$\boxed{V_1 = 100 \text{ V}}$$

$$-V_1 + 17V_2 = 240$$

$$\boxed{V_2 = 20 \text{ V}}$$

$$3) a) \frac{V_1 - V_2}{1250} + \frac{V_1}{1000} + 20 \cdot 10^{-3} = 0$$

$$2.75V_1 - V_2 = -25$$

$$\frac{V_2 - V_1}{1250} + \frac{V_2}{4000} + \frac{V_2}{2000} + \frac{V_2 + 2500i}{200} = 0$$

$$r = \frac{V_2 - V_1}{1250}$$

$$26.2V_2 - 3.2V_1 - 50000i = 0$$

$$-13.8V_2 + 3L.8V_1 = 0$$

$$V_1 = 60 \quad V_2 = 160$$

$$i = \frac{160 - 60}{1250} = 0.08 A$$

$$P_{2000k} = V_1 \cdot 20 \cdot 10^{-3} = 1.2 W$$

$$P_{2500i} = 2500i \cdot i = 2500(0.08) \cdot \left(\frac{160 - 2500(0.08)}{200}\right)$$

$$= \boxed{40W}$$

$$b) \sum P = \frac{V_1^2}{1000} + 1250i^2 + \frac{V_2^2}{4000} + \frac{V_2^2}{2000} + i^2 200$$

$$= 28.8 W$$

$$38.8 + 1.2 = \boxed{40W}$$

$$4) \quad 7 + \frac{V_0}{3} + \frac{V_0 - V_1}{1} = 0 \quad V_1 = \frac{4V_0 + 21}{3}$$

$$V_x = V_1 - 4 \quad \frac{V_1 - 4}{2} + \frac{V_1 - V_0}{1} - 2V_x = 0$$

$$-V_1 - 2V_0 + 12 = 0$$

$$-V_1 + 2V_0 + 12 = 0 \quad -\left(\frac{4V_0 + 24}{3}\right) - 2V_0 + 12 = 0$$

$$-4V_0 - 24 - 6V_0 + 36 = 0$$

$V_0 = 1.5 \text{ V}$

5)

$$V_1 - V_2 = 35i_0$$

$$V_1 = 35i_0 + V_2 \quad i = \frac{20 + V_d}{40}$$

$$-\frac{V_d}{1} + \frac{20 - V_d}{40} + \frac{20 - V_d - V_2}{4} = 0$$

$$\frac{V_1}{20} + \frac{V_1 - 20}{2} + \frac{V_2}{80} + \frac{V_2 - (20 - V_d)}{4} + 3,125V_d = 0$$

$$\frac{35i_0 + V_2}{20} + \frac{35i_0 + V_2 - 20}{2} + \frac{V_2}{80} + \frac{V_2 - (20 - V_d)}{4} + 3,125V_d = 0$$

$$V_2 = -29 \text{ V} \quad V_d = 10 \text{ V}$$

$$V_1 = -20.25 \text{ V} \quad i_0 = 0.25 \text{ A}$$

$$P_{z=0} = V_d I_S$$

$$I_S = \frac{20 - V_1 + V_d}{1} = 30,125 \text{ A}$$

$$P = 20 \cdot 30,125 = \underline{\underline{602.5 \text{ W}}}$$

6)

$$53i_2 + 5(i_1 - i_3) + 3(i_1 - i_2) = 0$$

$$8i_1 - 3i_2 - 5i_3 + 53i_2 = 0$$

$$30i_2 - 3i_1 - 20i_3 = 30$$

$$27i_3 - 20i_2 - 5i_1 = 30$$

$$i_A = i_2 + i_3$$

$$8i_1 + 50i_2 - 58i_3 = 0$$

$$i_1 = 10 \text{ A} \quad i_2 = 32 \text{ A} \quad i_3 = 60 \text{ A}$$

$$i_1 = -8 \text{ A}$$

$$P = 53i_2 \cdot i_1 = 53(-8) \cdot 110 = \underline{-46640 \text{ W}}$$

7) a) $45i_{11} - 5i_{1e} - V_{zib} = 760$

$$10i_d - 10i_e + V_{zib} = 2160$$

$$-5i_{11} - 14i_d + 15i_e = 0$$

$$2i_b = i_d - i_{11} \quad i_b = i_e + i_{11}$$

$$i_{11} + i_d - 2i_e = 0$$

$$V_{zib} = 45i_{11} - 5i_e - 760$$

$$45i_{11} + 10i_d - 15i_e = 1000$$

$$\boxed{i_{11} = 26 \text{ A}}$$

$$\boxed{i_d = 10 \text{ A}}$$

$$\boxed{i_e = 18 \text{ A}}$$

$$\boxed{i_d = -7 \text{ A}}$$

$$\boxed{i_b = -8 \text{ A}}$$

$$\boxed{i_c = 8 \text{ A}}$$

b) $P_{240V} = 240 \cdot -10 = -2400 \text{ W}$

$$P_{4i_d} = 4(10) \cdot -14 = -720 \text{ W}$$

$$P_{2i_b} = 2(-8)(45(26) - 5(18) - 760) = -5120 \text{ W}$$

$$V_{10A} + 40i_a = 280 \text{ V}$$

$$P_{10A} = 280 \cdot 19 = \underline{5320 \text{ W}}$$

$$P_{dev} = -520 - 720 - 2400 = -8240 \text{ W}$$

$$P_{dB} = 2170 \text{ W} + 5320 = 8240$$

$$P_{dev} = P_{dB} = 8240$$

8) a) Node analysis as there are less constraints

$$b) I_6 = \frac{V_1}{250} \quad I_4 = \frac{V_1}{100} \quad I_1 = 200 \text{ mA} - I_6$$

$$V_1 = V_a - 20$$

$$I_1 = I_4 + 0.003 V_A$$

$$I_2 = \frac{V_A}{500}$$

$$V_a = 44 \text{ V} \quad V_B = -72 \text{ V}$$

$$I_1 = 200 \text{ mA} - \frac{V_1}{250} = 0.2 - \frac{V_A}{250} = 0.024 \text{ A}$$

$$20 \cdot 0.024 = \underline{\underline{480 \text{ mW}}}$$

$$9) a) i_1 = \frac{120}{240 \text{ k}} = 3 \text{ mA} \quad R_1 = \frac{(40 \text{ k})(60 \text{ k})}{100 \text{ k}} = 24 \text{ k}\Omega$$

$$V_1 = (3)(24) = 72 \text{ V} \quad R_2 = 24 \text{ k} + 4 \text{ k} + 2 \text{ k} = 30 \text{ k}\Omega$$

$$i_2 = \frac{72}{300} = 2.4 \text{ mA} \quad R_3 = \frac{(30)(90)}{120} = 22.5 \text{ k}\Omega$$

$$i_3 = 8.4 - 2.4 = 6 \text{ mA} \quad V_3 = 6 \cdot 22.5 = 135 \text{ V}$$

$$i_0 = \frac{135}{40 \text{ k}} = -3.375 \text{ mA}$$

$$6) V_1 = (-3.375 \text{ m})(2.5k + 15k) = -59.0625 \text{ V}$$

$$i_2 = \frac{V_1}{90} = \frac{-59.0625}{90k} = -0.6563 \text{ mA}$$

$$i_x = 8.4 + i_2 - 3.375 = 4.3687 \text{ mA}$$

$$V_2 = i_x(4+2) + V_1 = -32.8503 \text{ V}$$

$$i_w = \frac{V_2}{60} = -0.5475 \text{ mA}$$

$$i_y = i_w + i_x = 3.8212 \text{ mA}$$

$$P = (120)(i_y) = \boxed{10.4585 \text{ W}}$$

$$10) \text{ a) } V_1 = 2 \cdot 6 = 12 \text{ V}$$

$$V_2 = (1)(5) = 5 \text{ V}$$

$$I_1 = \left(\frac{17}{17}\right) = 1 \text{ A} \quad I_2 = \left(\frac{34}{17}\right) = 2 \text{ A}$$

$$\left(\frac{1}{17} + \frac{1}{17}\right)^{-1} = 8.5 \text{ m} \quad I_b = -\left(\frac{8.5}{16}\right) = \boxed{1 - 0.85 \text{ A}}$$

$$\text{b) } 6(i_a - 2) + 6i_1 + 5(i_a - 1) + 17(i_a - i_b) - 3i_c = 0$$

$$i_a = \frac{5i_1 + 17i_b}{34}$$

$$-17i_a + 14.5i_b = -34$$

$$i_b = -\frac{281}{340} \Rightarrow \boxed{i_b = -0.85 \text{ A}}$$