

Santa Clara University

Department of Electrical and Computer Engineering

No. _____

DAREN LIU

Submitted on:

10/1/20

Name (please print)

- Include this page with Homework

- Write Name and Page Number on each page

ELEN 153
Fall 2020

Problem Set #1

Due: 10-01-2020, Thursday, 12:00 pm

1. A silicon nFET is fabricated with the following specification:

Threshold voltage = 0.7 V; Process transconductance = $154 \mu\text{A/V}^2$; Width = 20 μm ; Channel length = 47 nm.

(10) i) Calculate the Device transconductance of the nFET.

(42) ii) Indicate Threshold voltage, V_{Tn} , Saturation voltage, V_{sat} , Gate-Source voltages, V_{GSn} , and Drain-Source voltages, V_{DSn} in the I_{Dn} - V_{GSn} and I_{Dn} - V_{DSn} Figs. (see back) to verify if Channel is ON/OFF, mode of operation (saturation/non-saturation), and then calculate and indicate the magnitude of Drain current, I_{Dn} for the operating Gate-Source V_{GSn} and Drain-Source V_{DSn} voltages in the Table below. Show all calculations for each case separately.


Operation Point	V_{GSn} (V)	V_{DSn} (V)	If $V_{GSn} \geq V_{Tn}$ → Channel ON If $V_{GSn} < V_{Tn}$ → Channel OFF	$V_{sat} = V_{GSn} - V_{Tn}$ (V)	If $V_{DSn} \geq V_{sat}$ → Saturation If $V_{DSn} < V_{sat}$ → Non-Saturation	Drain Current (mA)
a	1.25	0.51				
b	0.65	2.13				
c	1.94	1.87				
d	0.76	0.82				

2. The nFET in Figure has power supply voltage = 3.3 V and

(8) Threshold voltage = 0.65 V. Find the output voltage, V_{out} for input voltages, $V_{in} = 2.58 \text{ V}; 2.71 \text{ V}; 2.10 \text{ V}; 1.20 \text{ V}$.

If nFET is OFF, find V_{out} for minimum ON $V_{GSn} = V_{Tn}$.

Hint: Use Table below.

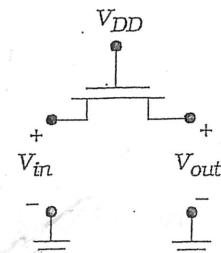


Let $V_{Gn} = V_{DD}$ (V)	Let $V_{in} = V_{Dn}$ (V)	Assume Channel ON $V_{Sn} = V_{Dn}$ (V)	$V_{GSn} = V_{Gn} - V_{Sn}$ (V)	If $V_{GSn} \geq V_{Tn}$ → Channel ON $V_{out} = V_{Sn}$ (V)	If $V_{GSn} < V_{Tn}$ (V) → Channel OFF Assume $V_{Gn} - V_{Sn} = V_{GSn} = V_{Tn}$ $V_{Sn} = V_{Gn} - V_{Tn} = V_{out}$

3. Consider the two-nFET chain in Figure. The power supply voltage = 5.0 V and Threshold voltage is 0.5V. Find the output voltage V_{out}

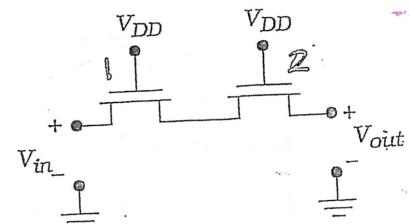(16) for $V_{in1} = 4.55 \text{ V}; 3.18 \text{ V}; 4.69 \text{ V}; 2.90 \text{ V}$. If nFETs are OFF, find V_{Sn1} or V_{out} for minimum ON V_{GSn1} and $V_{GSn2} = V_{Tn}$.

Hint: Use Table in Problem 2 above to find V_{Sn1} , then use a second Table with $V_{Sn1} = V_{Dn2}$ to find V_{out} .




Next page →

4. The output of nFET1 is used to drive the gate of another nFET2 as shown in Figure. Assume power supply voltage = 4.0 V and Threshold voltage = 0.75 V.

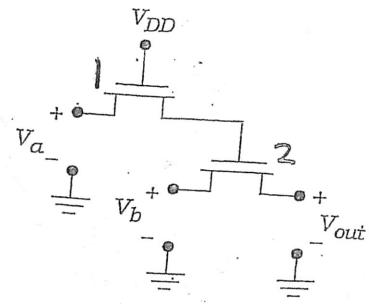- (16) Find V_{out} for input voltages $V_a = 2.5$ V, $V_b = 1.65$ V; $V_a = 3.6$ V, $V_b = 0.1$ V; $V_a = 1.9$ V, $V_b = 0.7$ V; and $V_a = 3.1$ V, $V_b = 0.3$ V. If nFETs are OFF, find V_{Sn1} and V_{out} for minimum ON V_{GSn1} and $V_{GSn2} = V_{Tn}$.


Hint: Repeat processes in Problem 2 with $V_{Gn2} = V_{Sn1}$.




5. The pFET in Figure has gate voltage = 0 V and Threshold voltage = -0.8 V. Find V_{out} for the input

- (8) Voltages, $V_{in} = 1.6$ V; 0.7 V; 2.1 V; 0.3 V. If pFET is OFF, find V_{out} for minimum ON $V_{SGp} = |V_{Tp}|$

Hint.: Use Table below.


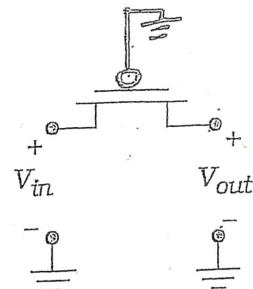


$V_{Gp} = 0$	Let $V_{in} = V_{Dp}$	Assume Channel ON $V_{Sp} = V_{Dp}$	$V_{SGp} = V_{Sp} - V_{Gp}$	If $V_{SGp} \geq V_{Tp} $ → Channel ON $V_{out} = V_{Sp}$	If $V_{SGp} < V_{Tp} $ → Channel OFF Assume $V_{Sp} - V_{Gp} = V_{SGp} = V_{Tp} $ $V_{Sp} = V_{Gp} + V_{Tp} = V_{out}$
--------------	-----------------------	--	-----------------------------	--	---

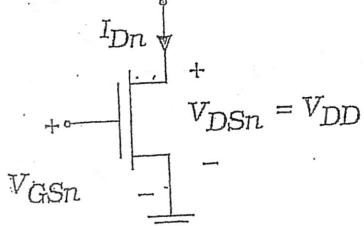

$$I_{Dn} = \frac{\beta_n}{2} [2(V_{GSn} - V_{Tn})V_{DSn} - V_{DSn}^2]$$
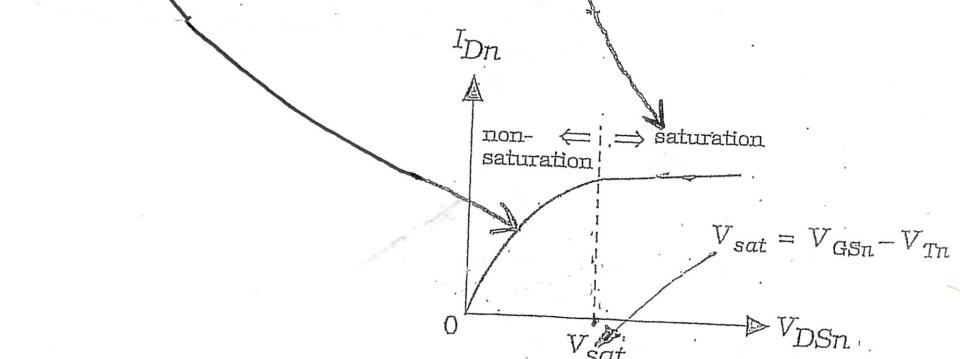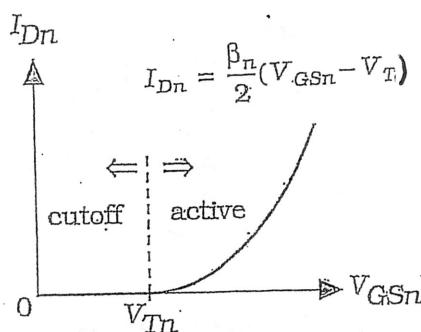
$$I_{Dn} = \frac{\beta_n}{2} (V_{GSn} - V_{Tn})^2$$



$$1) \text{ i) } V_{Tn} = 0.7 \text{ V} \quad K_n' = 154 \text{ mA/V}^2 \quad W = 20 \mu\text{m} \quad L = 47 \text{ nm} \quad \text{Daren Liu ①}$$

$$B_n = K_n' \left(\frac{W}{L} \right)$$

$$= (154) \left(\frac{20 \cdot 10^{-6}}{47 \cdot 10^{-9}} \right) = 65531.91 \text{ mA/V}^2 = 6.55 \cdot 10^{-2} \frac{\text{A}}{\text{V}^2}$$

ii)

$$\text{a) } V_{GSn} = 1.25 \quad V_{DSn} = 0.5 \mid V_{Tn} = 0.7$$

$$V_{GSn} \geq V_{Tn}: 1.25 \geq 0.7, \text{ Channel ON}$$

$$V_{sat} = V_{GSn} - V_{Tn} = 1.25 - 0.7 = 0.55 \text{ V}$$

$$V_{DSn} < V_{sat}: 0.5 < 0.55, \text{ Non-saturation}$$

$$I_{Dn} = \frac{B_n}{2} (2(V_{GSn} - V_{Tn}) V_{DSn} - V_{DSn}^2)$$

$$= \frac{6.55 \cdot 10^{-2}}{2} (2(0.55)(0.5)) - (0.5)^2 = 9.86 \cdot 10^{-3} \text{ A}$$

$$\text{b) } V_{GSn} = 0.65, \quad V_{DSn} = 2.13$$

$$V_{GSn} < V_{Tn}: 0.65 < 0.7, \text{ Channel OFF}$$

$$V_{sat} = V_{GSn} - V_{Tn} = 0.65 - 0.7 = -0.5 \text{ V}$$

$$V_{DSn} \geq V_{sat}: 2.13 \geq -0.5, \text{ Saturation}$$

$$I_{Dn} = 0 \text{ A}$$

$$\text{c) } V_{GSn} = 1.94 \quad V_{DSn} = 1.87$$

$$V_{GSn} \geq V_{Tn}: 1.94 \geq 0.7, \text{ Channel ON}$$

$$V_{sat} = V_{GSn} - V_{Tn} = 1.94 - 0.7 = 1.24 \text{ V}$$

$$V_{DSn} \geq V_{sat}: 1.87 \geq 1.24, \text{ Saturation}$$

$$I_{Dn} = \frac{6.55 \cdot 10^{-2}}{2} (1.94 - 0.7)^2 = 5.04 \cdot 10^{-2} \text{ A}$$

$$\text{d) } V_{GSn} = 0.76, \quad V_{DSn} = 0.82$$

$$V_{GSn} \geq V_{Tn}: 0.76 \geq 0.7, \text{ Channel ON}$$

$$V_{S_{\text{sat}}} = V_{G_{\text{on}}} - V_{T_n} = 0.76 - 0.7 = 0.7 \text{ V}$$

Daren Liu ②

$$V_{D_{\text{SN}}} \geq V_{S_{\text{sat}}} : 0.82 \geq 0.7, \text{ Saturation}$$

$$I_{Dn} = \frac{k_n}{2} (V_{G_{\text{on}}} - V_{T_n})^2 = \frac{6.55 \cdot 10^{-2}}{2} (0.76 - 0.7)^2 = 1.18 \cdot 10^{-4} \text{ A}$$

2) $V_{DD} = 3.3 \text{ V}$ $V_{T_n} = 0.65$

$$V_{in} = 2.58) \quad V_{G_n} = 3.3 \quad V_{Dn} = 2.58 \quad \text{Assume ON: } V_{sn} = 2.58$$

$$V_{G_{\text{SN}}} = V_{G_n} - V_{sn} = 3.3 - 2.58 = 0.72$$

$$V_{G_n} \geq V_{T_n} : 0.72 \geq 0.65, \text{ Channel ON}$$

$$V_{out} = V_{sn} = 2.58 \text{ V}$$

$$V_{in} = 2.71) \quad V_{G_n} = 3.3 \quad V_{Dn} = 2.7 \quad \text{Assume ON: } V_{sn} = 2.7$$

$$V_{G_{\text{SN}}} = V_{G_n} - V_{sn} = 3.3 - 2.7 = 0.6$$

$$0.6 < 0.65, \text{ Channel OFF}$$

$$V_{G_n} - V_{sn} = V_{G_{\text{SN}}} = 0.65$$

$$3.3 - V_{sn} = 0.65 \quad V_{sn} = 2.65$$

$$V_{out} = V_{sn} = 2.65 \text{ V}$$

$$V_{in} = 2.10) \quad V_{G_n} = 3.3 \quad V_{Dn} = 2.10 \quad \text{Assume ON: } V_{sn} = 2.10$$

$$V_{G_{\text{SN}}} = 3.3 - 2.10 = 1.2$$

$$V_{G_{\text{SN}}} \geq V_{T_n} : 1.2 \geq 0.65, \text{ Channel ON}$$

$$V_{out} = 2.10 \text{ V}$$

$$V_{in} = 1.20) \quad V_{G_n} = 3.3 \quad V_{Dn} = 1.20 \quad \text{Assume ON: } V_{sn} = 1.2$$

$$V_{G_{\text{SN}}} = 3.3 - 1.2 = 2.1$$

$$V_{G_{\text{SN}}} \geq V_{T_n} : 2.1 \geq 0.65, \text{ Channel ON}$$

$$V_{out} = 1.2 \text{ V}$$

Daren Liu ③

3) $V_{DD} = 5 \quad V_{Tn} = 0.5$

$$V_{in_1} = 4.55 \rightarrow 1) V_{Gn_1} = 5 \quad V_{Dn_1} = 4.55 \quad V_{sn_1} = 4.55$$

$$V_{Gn_1} = 5 - 4.55 = 0.45$$

$$V_{Gsn_1} < V_{Tn} : 0.45 < 0.5, nFET_1 \text{ is OFF}$$

$$V_{sn_1} = V_{Gn_1} - V_{Tn} = 4.50 \text{ V}$$

2) $V_{sn_1} = V_{Dn_2} = 4.5$

$$V_{sn_2} = V_{Dn_2} = 4.5$$

$$V_{Gsn_2} = 5 - 4.5 = 0.5$$

$$V_{Gsn_2} \geq V_{Tn} : 0.5 \geq 0.5$$

$$V_{out} = V_{sn_2} = 4.5 \text{ V}$$

$V_{in} = 3.18 \rightarrow V_{Gn_1} = 5 \quad V_{Dn_1} = 3.18 \quad V_{sn_1} = 3.18$

$$V_{Gsn_1} = 5 - 3.18 = 1.82$$

$$V_{Gsn_1} \geq V_{Tn} : 1.82 \geq 0.5, nFET_1 \text{ is ON}$$

$$V_{Dn_2} = V_{sn_1} = 3.18$$

$$V_{sn_2} = 3.18$$

$$V_{Gsn_2} = 5 - 3.18 = 1.82$$

$$V_{out} = 3.18 \text{ V} \quad nFET_2 \text{ is ON}$$

$V_{in} = 4.69 \rightarrow V_{Gn_1} = 5 \quad V_{Dn_1} = 4.69 \quad V_{sn_1} = 4.69$

$$V_{Gsn_1} = 5 - 4.69 = 0.31$$

$$V_{Gsn_1} < V_{Tn} : 0.31 < 0.5, nFET_1 \text{ is OFF}$$

$$V_{sn_1} = 5 - 0.5 = 4.5$$

$$V_{Dn2} = V_{sn1} = 4.5$$

Durch Link (4)

$$V_{sn2} = V_{Dn2} = 4.5$$

$$V_{GSn2} = 5 - 4.5 = 0.5$$

$$V_{GSn2} \geq V_{Tn} : 0.5 \geq 0.5$$

$$V_{out} = 4.5 \text{ V}$$

$$V_{in} = 2.90) \quad V_{Gn} = 5 \quad V_{sn} = 2.1 \quad V_{Dn} = 2.9$$

$$V_{GSn} = 5 - 2.9 = 2.1$$

$$V_{GSn} \geq V_{Tn} : 2.1 \geq 0.5 \quad n\text{FET}_1 \text{ is ON}$$

$$V_{out} = 2.9 \text{ V} \quad n\text{FET}_2 \text{ is ON}$$

$$4) \quad V_{DD} = 4 \quad V_{Tn} = 0.75$$

$$V_a = 2.5, \quad V_b = 1.65) \quad V_{Gn1} = V_{DD} = 4 \quad V_{in} = V_a = 2.5$$

$$V_{Dn1} = 2.5 \quad V_{sn1} = 2.5$$

$$V_{GSn1} = 4 - 2.5 = 1.5 \quad V_{GSn1} \geq V_{Tn} : 1.5 \geq 0.75 \quad n\text{FET}_1 \text{ is ON}$$

$$V_{out1} = V_{DD2} = 2.5$$

$$V_{Gn2} = V_{DD2} = 2.5 \quad V_{in2} = V_b = 1.65$$

$$V_{Dn2} = 1.65 \quad V_{sn2} = 1.65$$

$$V_{GSn2} = 2.5 - 1.65 = 0.85$$

$$V_{GSn2} \geq V_{Tn} : 0.85 \geq 0.75, \quad n\text{FET}_2 \text{ is ON}$$

$$V_{out2} = 1.65 \text{ V}$$

$$V_a = 3.6, \quad V_b = 0.1) \quad V_{Gn1} = 4 \quad V_{sn1} = V_a = 3.6 \quad V_{Dn1} = 3.6$$

$$V_{GSn1} = 4 - 3.6 = 0.4$$

$$V_{GSn1} < V_{Tn} : 0.4 < 0.75 \quad n\text{FET}_1 \text{ is OFF}$$

$$V_{out_1} = V_{Gn_1} - V_{Tn} = 4 - 0.75 = 3.25$$

Daren Liu (5)

$$V_{Gn_2} = V_{out_1} = 3.25$$

$$V_{sn_2} = 0.1 \quad V_{Dn_2} = 0.1$$

$$V_{Gsn_2} = 3.25 - 0.1 = 3.15$$

$$V_{Gsn_2} \geq V_{Tn}: 3.15 \geq 0.75$$

$$V_{out_2} = 0.1 \text{ V}$$

$$V_a = 1.9, V_b = 0.7) \quad V_{Gn_1} = 4$$

$$V_{sn_1} = V_a = 1.9$$

$$V_{Dn} = 1.9$$

$$V_{Gsn_1} = 4 - 1.9 = 2.1$$

$$V_{Gsn_1} \geq V_{Tn}: 2.1 \geq 0.75 \quad n\text{FET}_1 \text{ is ON}$$

$$V_{out_1} = V_{sn_1} = 1.9$$

$$V_{Gn_2} = V_{out_1} = 1.9$$

$$V_{sn_2} = 0.7$$

$$V_{Dn_2} = 0.7$$

$$V_{Gsn_2} = 1.9 - 0.7 = 1.2$$

$$V_{Gsn_2} \geq V_{Tn}: 1.2 \geq 0.75 \quad n\text{FET}_2 \text{ is ON}$$

$$V_{out_2} = 0.7 \text{ V}$$

$$V_a = 3.1, V_b = 0.3) \quad V_{Gn} = 4 \quad V_{Dn_1} = V_a = 3.1 \quad V_{sn_1} = 3.1$$

$$V_{Gsn_1} = 4 - 3.1 = 0.9$$

$$V_{Gsn_1} \geq V_{Tn}: 0.9 \geq 0.75, n\text{FET}_1 \text{ is ON}$$

$$V_{out} = V_{sn_1} = 3.1$$

$$V_{Gn_2} = 3.1 \quad V_{Dn_2} = 0.3 \quad V_{sn_2} = 0.3$$

$$V_{Gsn_2} = 3.1 - 0.3 = 2.8$$

$$V_{Gsn_2} \geq V_{Tn}: 2.8 \geq 0.75, n\text{FET}_2 \text{ is ON}$$

$$V_{out_2} = 0.3 \text{ V}$$

$$5) V_{GP} = 0 \quad V_{TP} = -0.8$$

$$V_{in} = 1.6) \quad V_{DP} = V_{in} = 1.6 \text{ V} \quad V_{SP} = V_{DP} = 1.6$$

$$V_{SGP} = 1.6 - 0 = 1.6 \text{ V}$$

$$V_{SGP} \geq |V_{TP}| : 1.6 \geq 0.8, \text{ Channel ON}$$

$$V_{out} = 1.6 \text{ V}$$

$$V_{in} = 0.7) \quad V_{DP} = 0.7 \text{ V} \quad V_{SP} = V_{DP} = 0.7$$

$$V_{SGP} = 0.7 - 0 = 0.7$$

$$V_{SGP} < |V_{TP}| : 0.7 < 0.8 \quad \text{Channel OFF}$$

$$V_{out} = V_{SP} = V_{GP} + |V_{TP}| = 0 + 0.8 = 0.8 \text{ V}$$

$$V_{in} = 2.1) \quad V_{DP} = 2.1 \text{ V} \quad V_{SP} = 2.1$$

$$V_{SGP} = 2.1 \quad V_{SGP} \geq |V_{TP}| : 2.1 \geq 0.8 \quad \text{Channel ON}$$

$$V_{out} = V_{SP} = 2.1 \text{ V}$$

$$V_{in} = 0.3) \quad V_{DP} = 0.3 \text{ V} \quad V_{SP} = 0.3$$

$$V_{SGP} = 0.3 \quad V_{SGP} < |V_{TP}| : 0.3 < 0.8 \quad \text{Channel OFF}$$

$$V_{out} = V_{SP} = |V_{TP}| = 0.8 \text{ V}$$