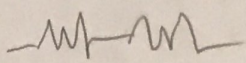
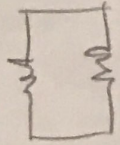
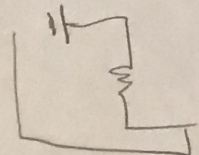


HW 2

1) A series <sup>circuit</sup> means that 2 or more resistors are positioned consecutively. 

A parallel circuit means that 2 or more resistors are parallel to each other but are not in series. 

An open circuit is where the resistance of a circuit is  $\infty$ . 

A short circuit is where the resistance between two nodes is zero.

A ground node is where the voltage is 0V.

2) a) 6V

$$V_{AB} = -6$$

$$I_A = 15 \cdot 10^{-3} \text{ A}$$

$$\alpha = -\frac{6}{15 \cdot 10^{-3}} \frac{\text{V}}{\text{A}}$$

b)  $P = V \times I$


$$I = 15 \cdot 10^{-3} \text{ A}$$

$$V = 6 \text{ V}$$

$$P = 0.09 \text{ W}$$



### c) Absorbmy

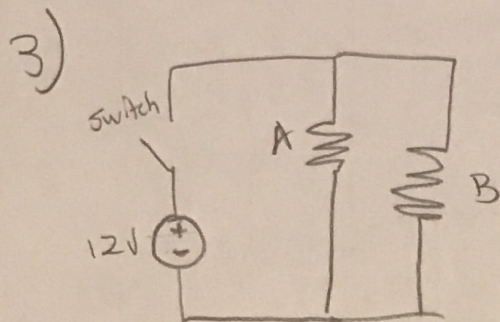

The battery can represent the voltage source.

The lamps can represent resistors.

The switch can represent a switch.

4)  $P = IV$      $V = IR$      $I = \frac{V}{R}$


$$P = \frac{V^2}{R}$$

$$V = -9$$

$$P = 640 \cdot 10^{-3} \text{ W}$$

$$R = \frac{V^2}{P} = \frac{64}{(640 \cdot 10^{-3})} = 100 \Omega$$

5)  $i_o = 2 \text{ A}$

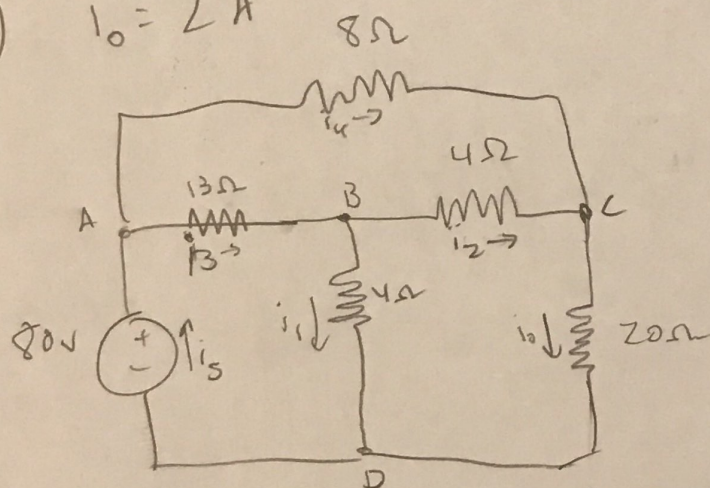

$$V = IR$$

ABDA  $-80 + 13i_3 + 4i_4 = 0$      $4i_1 + 13i_3 = 80$

BCDA  $4i_2 + 20i_o - 4i_1 = 0$      $4i_1 - 4i_2 = 40$

ACBA  $8i_4 - 4i_2 - 13i_3 = 0$

ACDA  $-80 + 8i_4 + 40 = 0$      $8i_4 = 40$

$$\boxed{i_4 = 5 \text{ A}}$$



Node C

$$-i_4 - i_2 + i_0 = 0$$

$$i_0 = i_4 + i_2$$

$$2 = 5 + i_2$$

$$\boxed{i_2 = -3 \text{ A}}$$

$$8(40) - 4(-3) - 13i_3 = 0$$

$$320 + 12 - 13i_3 = 0$$

$$4i_1 + 12 = 40$$

$$\boxed{i_1 = 7 \text{ A}}$$

$$7(4) + 13(i_3) = 80$$

$$\boxed{i_3 = 4 \text{ A}}$$

Node A

$$i_5 = i_4 + i_3 = 4 + 5 = 9$$

$$b) P_{13\Omega} = I_3^2 R = (16)(13) = 208 \text{ W}$$

$$P_{4\Omega} = (-3)^2(4) = 36 \text{ W}$$

$$P_{20\Omega} = (2)^2(20) = 80 \text{ W}$$

$$P_{8\Omega} = (5)^2(8) = 200 \text{ W}$$


$$c) P_{90V} = 80 \cdot i_5 = 80 \cdot 9 = 720 \text{ W}$$

$$P_{dis} = P_{13\Omega} + P_{4\Omega} + P_{20\Omega} + P_{8\Omega} = 208 + 36 + 200 + 80 \\ = 720 \text{ W}$$

$$P_{90V} = P_{dis}$$



6) a)

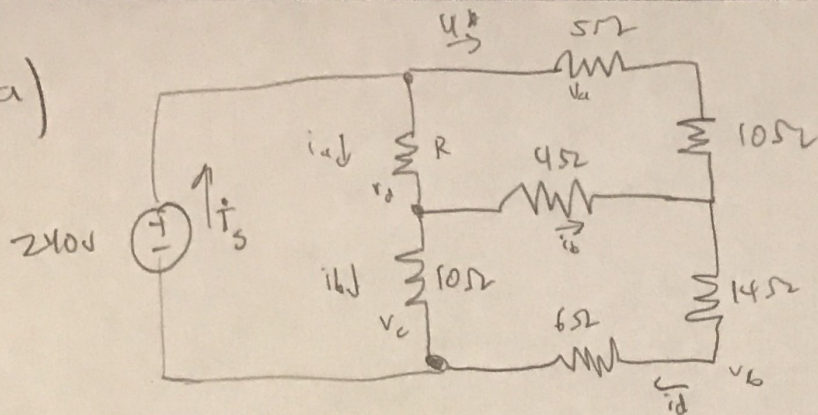

$$V = IR$$

$$V_d = (4)(5) = 4(5) = 20V$$

$$-240 + V_d + V_b = 0 \Rightarrow V_b = 180V$$

$$i_b = \frac{V_b}{14+6} = \frac{180}{20} = 9A$$

$$i_d = i_b + 4 = 9 + 4 = 13A$$

$$-V_c + 4i_b + V_b = 0$$

$$V_c = 4i_b + V_b = 4(9) + 180 = 216V$$

$$V_d = 240 - V_c = 240 - 216 = 24V$$

$$i_c = \frac{V_c}{10} = \frac{216}{10} = 21.6A$$

$$i_a = i_b + i_c = 9 + 21.6 = 30.6A$$

$$R = \frac{V_d}{i_a} = \frac{24}{30.6} = 0.784\Omega$$

b)  $i_c = i_a + 4 = 30.6 + 4 = 34.6A$

$$P_c = 240i_c = 240 \cdot 34.6 = 8304W$$



$$7) a) -12 + 2i + 5i_{\Delta} = 0 \quad 12 = 2i + 5i_{\Delta}$$

$$8i + 2i - 5i_{\Delta} = 0$$

$$10i = 5i_{\Delta}$$

$$2i = i_{\Delta}$$

$$12 = i_{\Delta} + 5i_{\Delta} = 6i_{\Delta}$$

$$i_{\Delta} = 2 \text{ A}$$

$$V_o = 2 \times i = 2 \text{ V}$$

$$b) I_1 = i_{\Delta} + i \quad (I = 1 + 8i_{\Delta})$$

$$= i_{\Delta} + i + 8i_{\Delta} = 9i_{\Delta} + i$$

$$i_{\Delta} = 2 \quad i = 1$$

$$I_1 = 19 \text{ A}$$

$$V_1 - 8 - V_o = 0 \quad V_1 = 10 \text{ V}$$

$$P_1 = 12 \cdot 19 = 228 \text{ W}$$

$$P_2 = V \times 8i = 8 \times 8 \cdot 2 = 128 \text{ W}$$

$$P_{\text{total}} = 356 \text{ W}$$

$$\frac{5\Omega}{P_1 = i_{\Delta}^2 \cdot R = (4) \cdot 5 = 20 \text{ W}}$$

$$\frac{2\Omega}{P_2 = 1 \cdot 2 = 2 \text{ W}}$$

$$\frac{2i}{P_3 = 2i \cdot I_1 = 2 \cdot 1 \cdot 19 = 38 \text{ W}}$$




$$P_4 = 8i \cdot I = 8 \cdot 1 \cdot 17 = 136 \text{ W}$$

$$P_5 = 8 \cdot i \cdot V_1 = 8 \cdot 2 \cdot 10 = 160 \text{ W}$$

$$P_{dis} = 20 + 2 + 38 * 136 + 160 = 356$$

8) a)

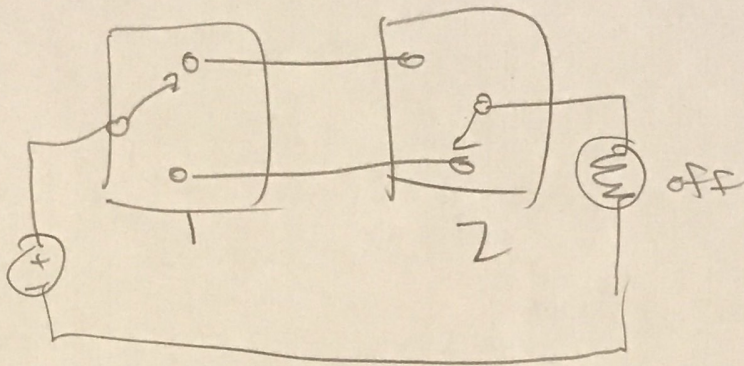

b)

