

HW 7

1) 14) $i_L(0^+) = i_o(0^-) = 4$

$$i_T = 4 \text{ A}$$

$$\frac{V_T}{I_T} = 0.25 \quad R_{th} = 0.25$$

$$\tau = \frac{L}{R} = \frac{5 \cdot 10^{-3}}{25} = 20 \text{ ms}$$

$$i_o = i_L(0^-) e^{-\gamma t} = 4 e^{-t/0.02} = 4 e^{-50t}$$

$$V_o = L \frac{di_o}{dt} = (5 \cdot 10^{-3}) \frac{d}{dt} (4 e^{-50t}) = \boxed{-4 e^{-50t}}$$

2) a) $i_{1.25H}(0^-) = i_{10H}(0^-) = -2 \text{ A}$

$$i_o(0^-) = 0 \text{ A}$$

$$L_{eq} = 1.25 + \frac{10 \cdot 6}{10+6} = 5 \text{ H}$$

$$\frac{1}{\tau} = \frac{R}{L} = \frac{7500}{5} = 1500$$

$$i_L(t) = i_o(0^-) e^{t/\tau} = 2 e^{-1500t} \text{ A}$$

$$V_o(t) = L \frac{di_o}{dt} = (3.75) \frac{d}{dt} (-2 e^{-1500t}) = 11250 e^{-1500t} \text{ V}$$

b) $i_o(+) = - \frac{1}{L} \int_0^+ V_o(t) dt + i_o(0^-) = - \frac{11250}{6} \left(\frac{e^{-1500t}}{-1500} \right) \Big|_0^+$

$$= 125(e^{-1500t} - 1) / 4$$

$$3) \text{ z6) a)} V(0^-) = \frac{12/168}{12/168 + 1,8} (-120) = -102 \text{ V}$$

$$V(t) = V(0^-) e^{-\frac{t}{RC}} = -102 e^{-25t} \text{ V}$$

$$P_{12\text{ k}\Omega} = \frac{(-102 e^{-25t})^2}{12600} = 0.867 e^{-50t} \text{ W}$$

$$W_{12\text{ k}\Omega} = \int_0^{0.012} 0.867 e^{-50t} dt = 7824 \text{ mJ}$$

$$\text{b)} W(0) = \frac{1}{2} \left(\frac{10}{2} \cdot 10^{-6} \right) (-102)^2 = 17340 \text{ mJ}$$

$$= \int_0^t P_{12\text{ k}\Omega} dt = \int_0^t 0.867 e^{-50t} dt = \\ 17340 (1 - e^{-50t}) \text{ mJ} \\ e^{-50t} = 1 - 0.25 \\ t = 27.73 \text{ ms}$$

$$4) \text{ z9) a)} V(0^-) = -18 \text{ V}$$

$$-V_f + 20000(i_t + \alpha V_A) + 5000 i_f = 0$$

$$V_A = 5000 i_f$$

$$R_{th} = \frac{V_f}{i_f} = 25000 + 1000 \cdot 10^6 \alpha$$

$$T = R_{th} C = 40 \text{ ns}$$

$$R_{th} = \frac{V_f}{i_f} = 50 \text{ k}\Omega$$

$$\alpha = \frac{50000 - 25000}{100 \cdot 10^6} = 0.25 \cdot 10^{-3} \text{ A/V}$$

$$b) v(t) = v(0^-) e^{-\frac{t}{T}} \approx -18 e^{-25+} V$$

$$\frac{V_A}{5000} + \frac{V_A - V(t)}{20000} + \alpha V_A = 0 = \frac{-18 e^{-25+}}{20000}$$

$$\boxed{V_A = -18 e^{-25+} V}$$

$$5) 44) i_L(0^-) = i_L(0^+) = 15 mA$$

$$\frac{V_A}{15} + \underbrace{\frac{V_A - V_o(0^+)}{5}}_{= 20 \cdot 10^{-3}} = 20 \cdot 10^{-3}$$

$$V_A = 0.75 V_o(0^+) + 0.075$$

$$i_A = \frac{V_o(0^+)}{40} + 0.005$$

$$V_o(0^+) = -0.08 = -80 mV$$

$$V_o(\infty) = 0$$

$$i_A = \frac{V_T}{8} - q i_A \quad i_D = \frac{V_T}{80}$$

$$i_T = \frac{V_T}{20} + \frac{V_T}{8} - q i_A$$

$$\frac{i_T}{V_T} = \frac{1}{16} \quad \frac{V_T}{i_T} = 16 \quad R_{th} = 16 \Omega$$

$$T = \frac{L}{R_{th}} = \frac{4 \cdot 10^{-3}}{16} = 0.25 ms$$

$$V_o(t) = 0 + (-80) e^{-\frac{t}{0.25 \cdot 10^{-3}}} = -80 e^{-4000+} mV$$

$$6) \text{ ad)} \quad T = \frac{L_{02}}{R} = \frac{24 \cdot 10^{-3}}{120} = 0.2 \text{ ms}$$

$$i_L(\infty) = -50 \text{ mA}$$

$$i_L(t) = -50 + 75e^{-5000t} \text{ mA}$$

$$V_o = -9e^{-5000t} \text{ V}$$

$$\text{b)} \quad 0.4 \cdot (-50 + 75e^{-5000t} \text{ mA}) = -20 + 30e^{-5000t} \text{ mA}$$

$$\text{c)} \quad \cancel{0.6} \cdot (-50 + 75e^{-5000t}) = -30 + 45e^{-5000t} \text{ mA}$$

$$7) \text{ sv) a)} \quad V_o = 75 \frac{10}{10+5} = 50 \text{ V}$$

$$V_o(\partial) = -100 \cdot \frac{40}{50} = -80 \text{ V}$$

$$R_{eq} = 40 // 10 = 8 \text{ k}\Omega$$


$$T = 3.2 \cdot 10^{-4} = 0.32 \text{ ms}$$

$$V_o(t) = -80 + 130e^{-3125t} \text{ V}$$


$$\text{b)} \quad i_o(t) = \frac{-80 + 130e^{-3125t} + 100}{10 \cdot 10^3} =$$

$$2 + 13e^{-3125t} \text{ mA}$$

8) 6)

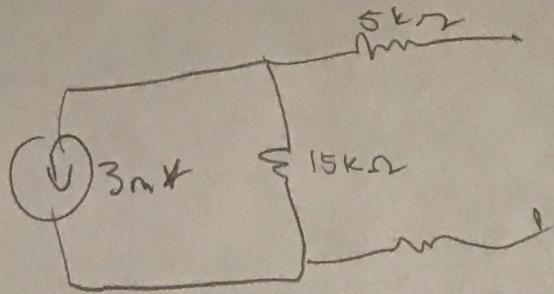
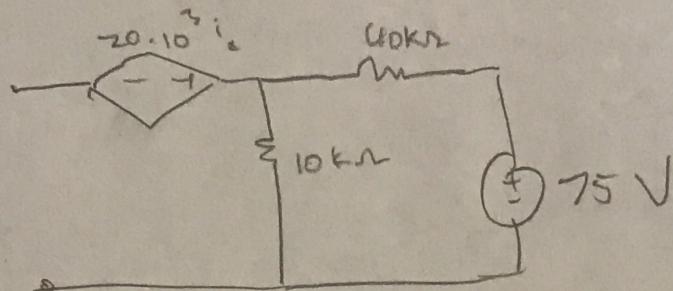
$$V(0^-) = (3 \cdot 10^{-3}) / (15 \cdot 10^3) \cdot 5 \cdot 10^3 = 45 \text{ V}$$




$$V_0(\infty) = -10 \cdot 10^3 \left(\frac{15 - 75}{40k} \right) + 15 = 30 \text{ V}$$

$$i_A = \frac{30}{10 + 40} i_+ = 0.2 i_+$$

$$V_T = (-10 \cdot 10^3) (0.2 i_+) + \left(\frac{(10)(40)}{50} \right) i_+ = -2000 i_+ + 8000 i_+ = 6000 i_+$$
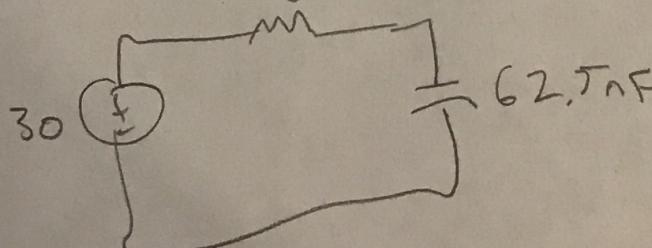
$$\frac{V_T}{i_T} = 6000 \quad R_{Th} = 6 \text{ k}\Omega$$



$$\begin{aligned} T &= (6 \cdot 10^3) (62.5 \cdot 10^{-9}) \\ &= -3.75 \cdot 10^{-4} \text{ s} \\ &= -3.75 \text{ ns} \end{aligned}$$

$$\begin{aligned} V_0(t+) &= 30 + (45 - 30) \left(e^{\frac{-t}{-3.75 \text{ ns}}} \right) \\ &= 30 + 15 e^{2.67 t} \end{aligned}$$

$$a) 63) V_c(0^+) = 0$$

$$i_b = 120 \frac{33000}{33000 + 47000} = 49.5 \text{ mA}$$

$$I_{L_P} = 1237.5 \text{ mA}$$

$$V_c(\infty) = -19.8 \text{ V}$$

$$t = RC = 4 \cdot 10^{-3} \text{ s} \approx 4 \text{ ms}$$

$$V_c(t) = -19.8 + 19.8 e^{-250t} \text{ V}$$

$$W(t) = 4.9 \cdot 10^{-5} \text{ J}$$

$$W(t_0) = 1.764 \cdot 10^{-5} \text{ J}$$

$$V_c^2(t_0) = -11.86 \text{ J}$$

$$-11.86 = -19.8 + 19.8 e^{-250t_0}$$

$$t_0 = 3.665 \text{ ms}$$

$$10) 65) a) V_{30nF}(+) = 120 \text{ V}$$

$$V_o(\infty) = 90 \frac{10}{60+120} = 30 \text{ V}$$

$$R_{eq} = \frac{60 \cdot 120}{60+120} = 40 \text{ k}\Omega$$

$$C_{eq} = \frac{30 \cdot 0.001}{90} = 20 \text{ nF}$$

$$\tau = 0.8 \text{ ms}$$

$$V_c(t) = 30 + 90 e^{-1250t} \text{ V}$$

$$b) -i_s + \frac{V_o}{60000} + \frac{V_o - 90}{120,000} = 0$$

$$i_s = 2.25 \cdot 10^{-3} \cdot e^{-1250t} \text{ A}$$

$$V_i(t) = \frac{1}{60 \cdot 10^{-3}} \left\{ 2.25 \cdot 10^{-3} e^{-1250x} \right\} dx =$$

$$30 - 30 e^{-1250t} \text{ V}$$