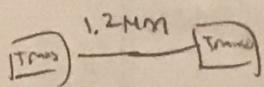


HW #1

1) 10 layers

Bottom layer transistors connected by copper lines

& others all copper lines



5 billion transistors
 $(5 \text{ billion} - 1)$ copper lines on bottom layer

$$(100 \text{ million})(0.2 \text{ nm}) = 20,000,000 \text{ nm} = \text{length of 1 adjacent layer}$$

$$\approx 20 \text{ m}$$

$$(5 \text{ billion} - 1)(1.2 \text{ nm}) = 5,999,999,998.8 \text{ nm} = \text{length of copper connecting transistors}$$

$$\approx 6000 \text{ m}$$


$$2(5,999,999,998.8) = 11,999,999,997.6 \text{ nm} = \text{length of copper in the upper 9 layers}$$

$$\approx 12,000 \text{ m}$$

$$9(20 \text{ m}) + (6000 \text{ m}) + 9(12,000 \text{ m}) = 180 + 6000 + 108000$$


$$= \underline{\underline{114,180 \text{ m total}}}$$

2)

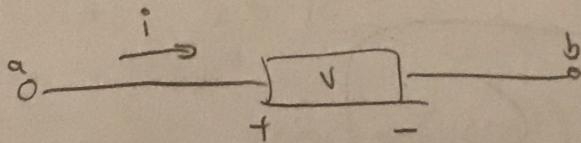

Passive sign convention shows that the circuit is absorbing power.

3) a)

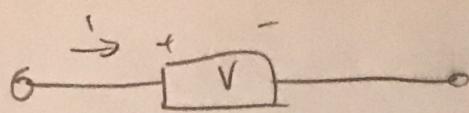

$$q(t) = \int i(t) dt = \int_0^t 125 e^{-2500t} \cdot 10^{-3} dt$$

$$= \int_0^{10^{-3}} 125 \{ e^{-2500t} dt = \int_0^{10^{-3}} 125 \{ -\frac{1}{2500} e^{-2500t} dt$$

$$= \frac{125 \cdot 10^{-3}}{-2500} \left. \int_0^t e^{-2500t} dt \right|_0^+ = -\frac{1}{20} \cdot 10^{-3} e^{-2500t} \Big|_0^+$$

$$= \boxed{\left(\frac{1}{20} \cdot 10^{-3} \left(e^{-2500t} - 1 \right) \right)_0^+}$$

$$b) \int_0^{\infty} \frac{1}{10 \cdot 10^{-3}} 125 e^{-2500t} dt = \frac{10^3}{20} \cdot \frac{1}{20} e^{-2500t} \Big|_0^{\infty} = -\frac{1}{20} (0 - 1)$$

$$-\frac{1}{20} \cdot 10^{-3} (0 - 1) = \boxed{\frac{1}{20} \cdot 10^{-3}}$$

$$c) q(0.0005) = -\frac{1}{20} \cdot 10^{-3} \left(e^{(-2500)(0.0005)} - 1 \right)$$

$$= \boxed{3.57 \cdot 10^{-5} C}$$

$$4) \text{ a) } i = 40 \text{ A} \quad V = 12$$

B should be absorbing power, so B.

$$\text{b) } 1.5 \text{ min} \cdot \frac{60 \text{ s}}{1 \text{ min}} = 90 \text{ s} \quad P = \frac{dW}{dt} = Vi$$

$$(12)(40) = W = \int_0^{90} 480 dt = (480)(90) = \boxed{43200 \text{ J}}$$

$$5) \quad V = 250 \cos 800\pi t \quad i = 8 \sin 800\pi t$$

$$\text{a) } P = V \cdot i = 250 \cos(800\pi t) \cdot 8 \sin(800\pi t)$$

$$= 2000 \cdot 0.5 [\sin(1600\pi t) + \sin(0)] = 1000 \sin(1600\pi t)$$

$$P_{\max} = \text{when } \sin(1600\pi t) = 1, \text{ so } \boxed{1000 \text{ W}}$$

$$\text{b) } P_{\text{delivered}} = P_{\text{absorbed}}$$

$$\boxed{1000 \text{ W}}$$

$$\text{c) } 2.5 \text{ ms} = 2.5 \cdot 10^{-3}$$

$$\frac{1}{2.5 \cdot 10^{-3}} \int_0^{2.5 \cdot 10^{-3}} 1000 \sin(1600\pi t) dt = \frac{1000}{2.5 \cdot 10^{-3}} \int_0^{2.5 \cdot 10^{-3}} \sin(1600\pi t) dt$$

$$= \frac{1000}{2.5 \cdot 10^{-3}} \left(-\frac{1}{1600\pi} \cos(1600\pi t) \right) \Big|_0^{2.5 \cdot 10^{-3}} = -\frac{1000}{1600\pi \cdot 2.5 \cdot 10^{-3}} + \frac{1000}{1600\pi \cdot 2.5 \cdot 10^{-3}} =$$


$$\boxed{0 \text{ W}}$$

$$d) \quad \frac{1}{15.625 \cdot 10^{-3}} \int_0^{15.625 \cdot 10^3} 1000 \sin(1600\pi t) dt = \frac{1000}{15.625 \cdot 10^{-3}} \int_0^{15.625 \cdot 10^3} \sin(1600\pi t) dt$$

$$= \left(\frac{1000}{15.625 \cdot 10^{-3}} \right) \left(-\frac{1}{1600\pi} \right) \cos(1600\pi t) \Big|_0^{15.625 \cdot 10^3} =$$

$$\left(\frac{1000}{15.625 \cdot 10^{-3}} \right) \left(-\frac{1}{1600\pi} \right) (-1 - 1) = \boxed{25.46 \text{ W}}$$

6) a) $P = V \cdot i$

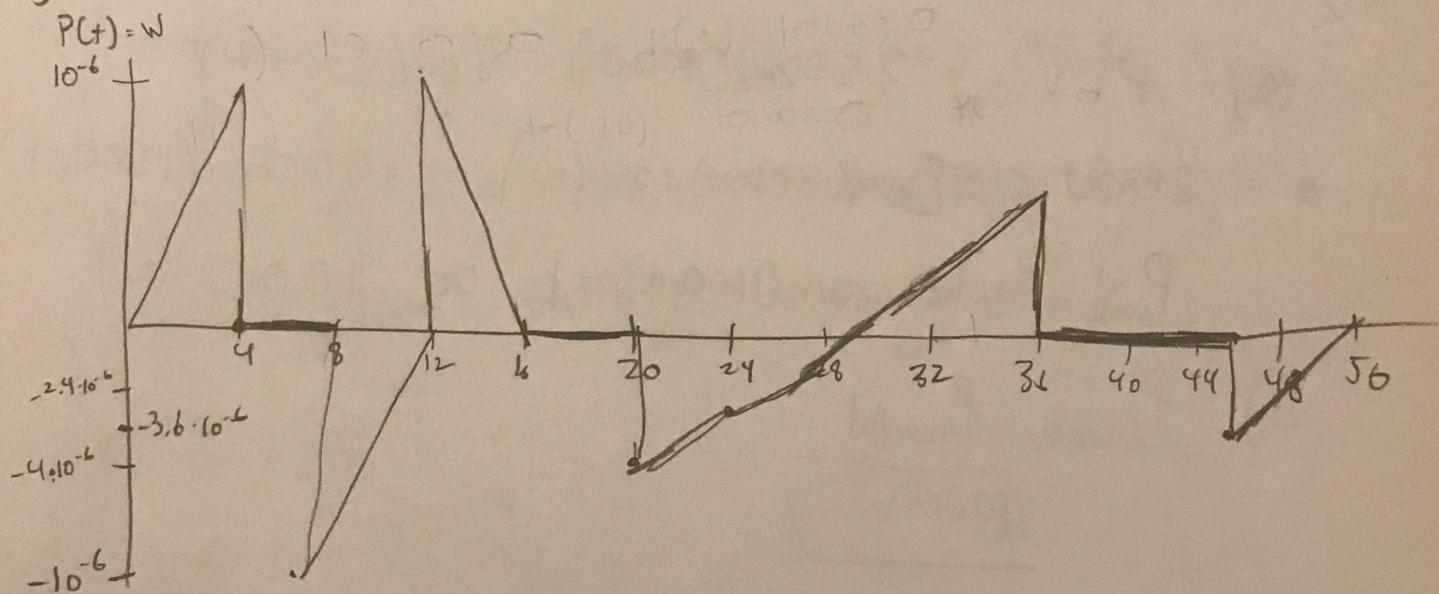

b) $P(4) = 0 \text{ W}$ $P(12) = 0 \text{ W}$

$P(36) = 0 \text{ W}$ $P(56) = 0 \text{ W}$

$$7) P_a = (-3)(-250) = -750$$

$$P_b = 4 \cdot 400 = 1600$$

$$P_c = -400$$

$$P_d = 150$$

$$P_e = -800$$

$$P_f = 200$$

$$P_a + P_c + P_e = -750 + 400 - 800 = 1950$$

$$P_b + P_d + P_f = 1600 + 150 + 200 = 1950$$

The circuit satisfies the power check

$$8) d = -1A$$

	V	X	P
a	120	-10	-1200
b	120	9	-1080
c	10	10	100
d	10	-1	10
e	-10	-9	90
f	-100	5	500
g	120	4	480
h	-220	-5	1100

$$P_a + P_b = P_{\text{developed}} = -2280.$$

$$P_c + P_d + P_e + P_f + P_g + P_h = P_{\text{absorbed}} = 2280.$$

$$P_{\text{developed}} = P_{\text{absorbed}}.$$